

## Design of Finite State Machines

### Steps involved in designing FSMs

1. Understand the description of the system. Usually, a timing diagram is helpful to consider different scenarios.
2. Construct the state/output table or the state diagram corresponding to the description.
3. Minimize number of identified states (optional, not required). The idea of minimization is to identify *equivalent states*. A pair of equivalent states can be replaced by a single state.

Two states  $S_1$  and  $S_2$  are equivalent if and only if two conditions are true:

1.  $S_1$  and  $S_2$  must produce the same values at the state-machine output(s).
2. For each *input combination*,  $S_1$  and  $S_2$  must have either the same next state or equivalent

4. State Assignment: Choose state variables to represent the states in the state table. For  $n$  states, the minimum number of variables you need is equal to  $\lceil \log_2 n \rceil$ . You may end up with *unused states*.

defines the # of FFs

- **Minimal risk:** Assumes the machine may get into unused states, and for any input combination, the unused states go to the "initial" state.

- **Minimal cost:** Assumes the machine will never enter an unused state. The next-state entries of the unused states can be marked as "don't-cares."

5. Assign binary codes to state variable. Examples: counting order, one-hot, almost one-hot, decomposed, ...


- **Counting order:** Simplest coding, however, it does not always lead to the simplest excitation equations, output equations, and or simplest logic circuits.

- **One-hot:** uses one bit per state. Therefore, it may require more number of state variables than the minimum ( $\lceil \log_2 n \rceil$ ). This approach usually leads to short excitation equations, since each FF must be set to 1 for transitions into only one state. But it also requires more number of FF than the minimum number.

- **Almost One-hot:** uses the "none-hot" combination for the initial state.

- **Gray Code:** one state variable changes on each state transition.

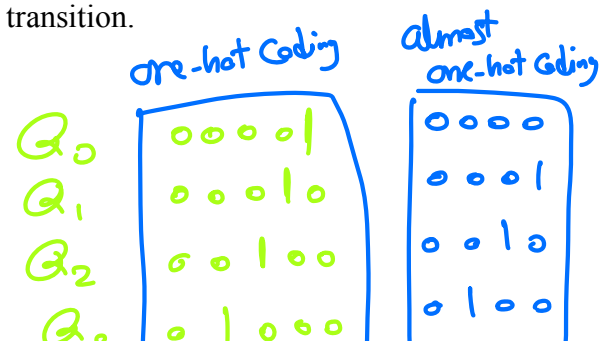- **Decomposed:** see Pages 463-464 in the textbook.






6. Substitute states in the state/output table with their assigned binary codes, to build the transition table.
7. Find FF characteristics equations, excitation and output equations. K-Maps could become useful here. If you use D FFs for state memory (the case in this course), you can easily obtain the excitation equations from the transition equations.
8. Draw the logic diagram.



**Example:** Design a state machine with two inputs, A and B, and a single output Z. Z is 1 if:

- A had the same value at each of the two previous clock ticks,
- or
- B has been 1 since the last time that the first condition was true

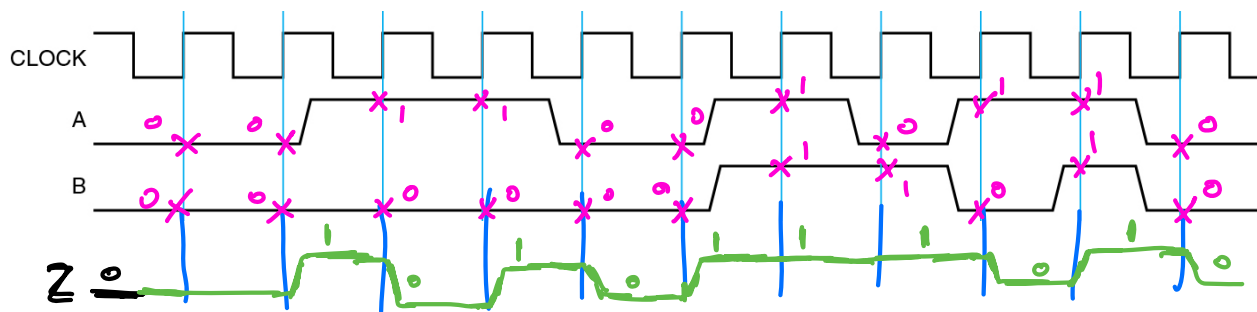**Step 1: Understand the description of the system.**



**Step 2: Construct the state/output table or the state diagram corresponding to the description.**

**INIT:** When the system powers up. The output Z will be 0 in this state.

**A0:** Got A = 0 on the previous tick,  $A \neq 0$  on the tick before that, and  $B \neq 1$  at some time since the previous pair of equal A inputs. The output Z will be 0 in this state.

**A1:** Got A = 1 on the previous tick,  $A \neq 1$  on the tick before that, and  $B \neq 1$  at some time since the previous pair of equal A inputs. The output Z will be 0 in this state.


**OK:** Got a pair of equal A inputs (0,0 or 1,1) on the previous two ticks. The output Z will be 1 in this state.

*Note:* When the system goes to OK state, it remains in the OK state if 1) A remains constant, or, 2)  $B=1$ . For the system to know if A has remained constant (when  $B \neq 1$ ), it needs to know its previous value of A. Therefore, we need to have two situations for the OK state:

**OK0:** the system got to this state with A0.

**OK1:** the system got to this state with A1.

INIT, A0, A1, 0K0, 0K1

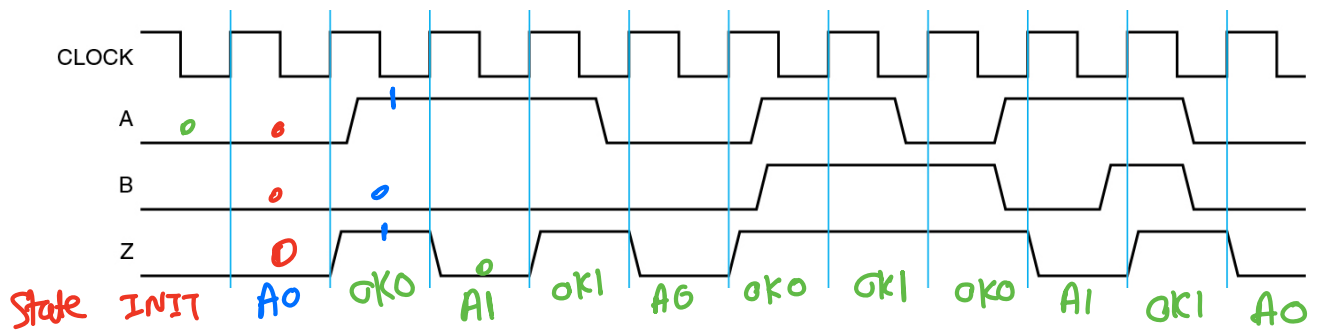


With these states, we can construct the state/output table:

	AB				Z
S	00	01	10	11	
INIT	A0	A0	A1	A1	0
A0	0K0	0K0	A1	A1	0
A1	A0	A0	0K1	0K1	0
0K0	0K0	0K0	A1	0K1	1
0K1	A0	0K0	0K1	0K1	1

$S^*$

State Diagram:

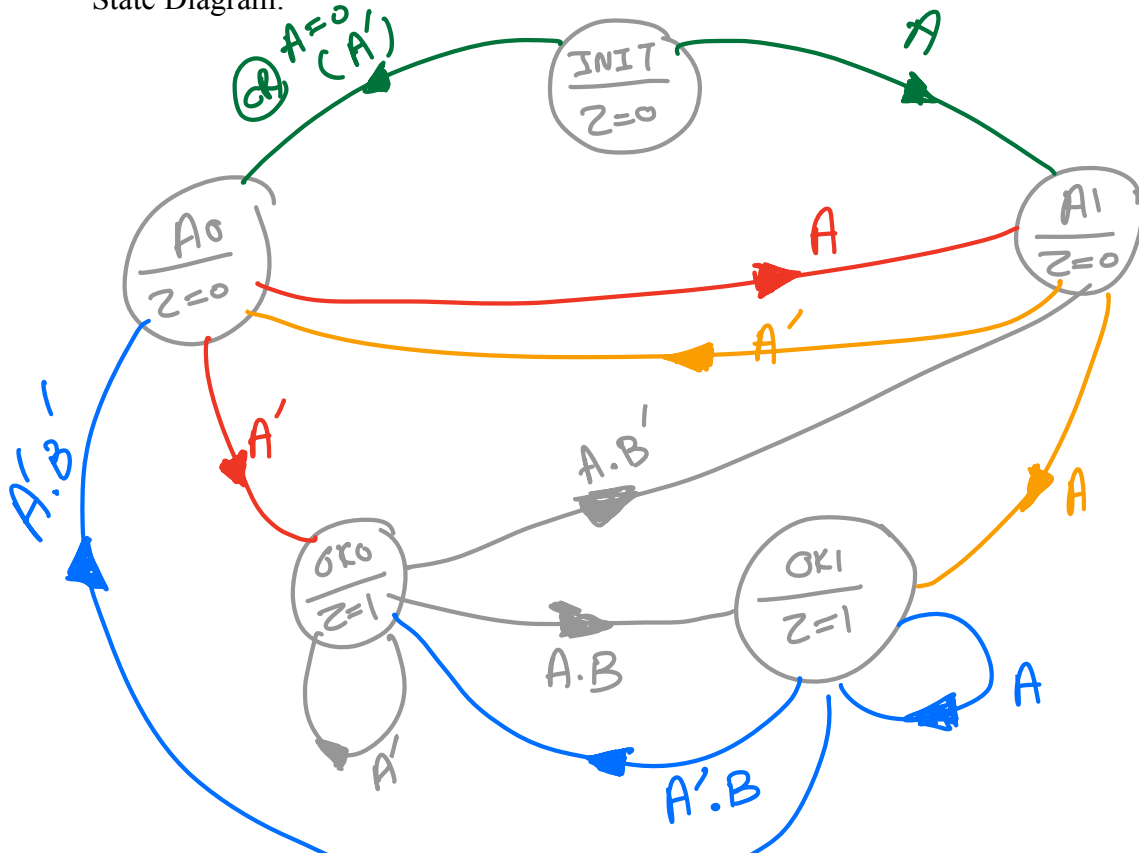

### Step 3: Minimize number of identified states (optional)

Meaning	S	A B				Z
		00	01	11	10	
Initial state	INIT	A0	A0	A1	A1	0
Got a 0 on A	A0	OK00	OK00	A1	A1	0
Got a 1 on A	A1	A0	A0	OK11	OK11	0
Got 00 on A	OK00	OK00	OK00	OKA1	A1	1
Got 11 on A	OK11	A0	OKA0	OK11	OK11	1
OK, got a 0 on A	OKA0	OK00	OK00	OKA1	A1	1
OK, got a 1 on A	OKA1	A0	OKA0	OK11	OK11	1

S\*

*Handwritten notes:*  
 - A blue box highlights the first four rows (INIT, A0, A1, OK00).  
 - Red arrows point from the 'Z' column to the text "equivalent states".  
 - A yellow box highlights the last three rows (OK00, OK11, OKA0, OKA1).

### Step 4: State Assignment: Choose state variables to represent the states in the state table.

5 states: INIT, A0, A1, OK0, OK1

To represent 5 states, we need at least 3 State variables

$$2^3 = 8 \text{ States} \rightarrow \boxed{3 \text{ unused States}}$$

Decomposed

### Step 5: Assign binary codes to state variable.

S	Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub>	Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub> Q <sub>4</sub> Q <sub>5</sub>	Q <sub>1</sub> Q <sub>2</sub> Q <sub>3</sub>
INIT	0 0 0	0 0 0 0 1	0 0 0
A0	0 0 1	0 0 0 1 0	1 0 0
A1	0 1 0	0 0 1 0 0	1 0 1
OK0	0 1 1	0 1 0 0 0	1 1 0
OK1	1 0 0	1 0 0 0 0	1 1 1

*Handwritten notes:*  
 - "Counting order" is written under the first three columns.  
 - "One-hot" is written under the next five columns.  
 - "Z (output)" is written under the last three columns.  
 - "Q<sub>3</sub> = 1 when A = 1" is written to the right of the last column.

Q<sub>1</sub> = 0 when S = INIT

Q<sub>1</sub> = 1 otherwise

$$Z = Q_1 \cdot Q_2 \cdot Q_3' + Q_1 Q_2 Q_3 = Q_1 \cdot Q_2 [Q_3' + Q_3] = Q_1 \cdot Q_2$$

Step 6: Substitute states in the state/output table with their assigned binary codes, to build the transition table.  
Using Decomposed Coding

S	AB				Z
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

$Q_1 Q_2 Q_3$

AB		00	01	11	10
100	100	101	101	101	101
110	110	101	101	101	101
100	100	111	111	111	111
110	110	111	111	111	111
100	100	111	111	111	111
110	110	111	111	111	111

$A, B, Q_1, Q_2, Q_3$

$Q_1^*, Q_2^*, Q_3^*$

$Q_1^*, Q_2^*, Q_3^*$

Step 7: Find excitation and output equations.

32-cell K-Map  
 $32 - 20 = 12$

$Q_1^* = Q_1 + Q_2 \cdot Q_3'$   
Unused States

$Q_1 = 0$

AB	00	01	11	10
$Q_2 Q_3$	1	1	1	1
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$Q_1 = 1$

AB	00	01	11	10
$Q_2 Q_3$	1	1	1	1
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$Q_2^* = Q_1 Q_3 \cdot A + Q_1 \cdot Q_3' \cdot A' + Q_1 \cdot Q_2 \cdot B$

$Q_1 = 0$

AB	00	01	11	10
$Q_2 Q_3$	0	0	0	0
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$Q_1 = 1$

AB	00	01	11	10
$Q_2 Q_3$	1	1	0	0
00	1	1	0	0
01	0	0	1	1
11	0	0	1	1
10	1	1	1	0

$Q_3^* = Q_1 \cdot A + A \cdot Q_2' \cdot Q_3'$

$Q_1 = 0$

AB	00	01	11	10
$Q_2 Q_3$	0	0	1	1
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$Q_1 = 1$

AB	00	01	11	10
$Q_2 Q_3$	0	0	1	1
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1


Taking the "minimal risk" approach, if the machine goes to

unused state, the next state will be "INIT" or


$$Q_1^* Q_2^* Q_3^* = 000$$

$$D_1 = Q_1^*, D_2 = Q_2^*, D_3 = Q_3^*$$


Step 8: Draw the logic diagram.

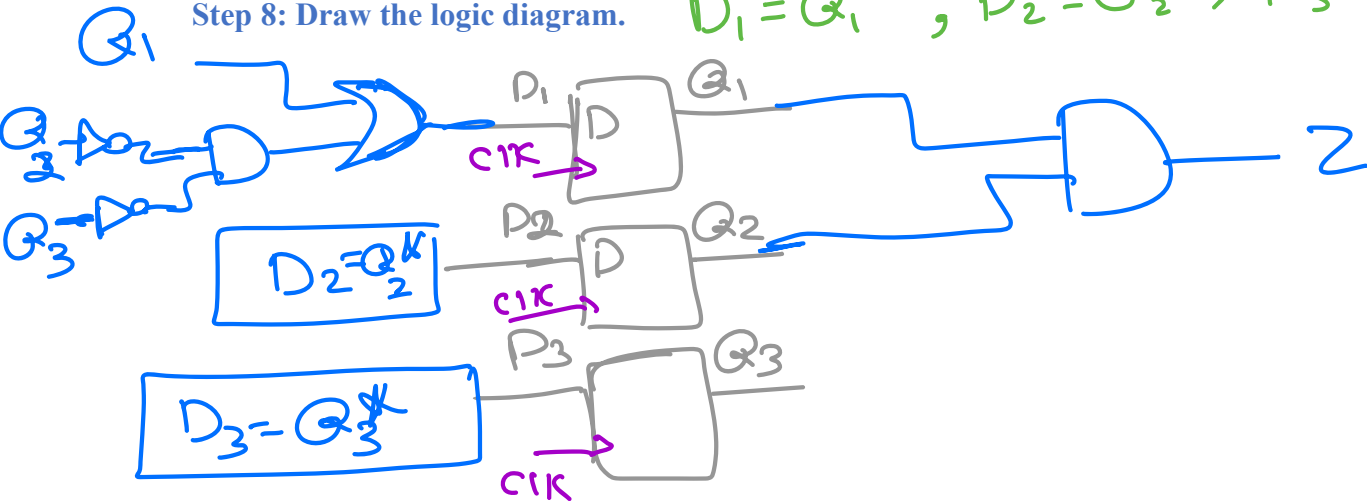

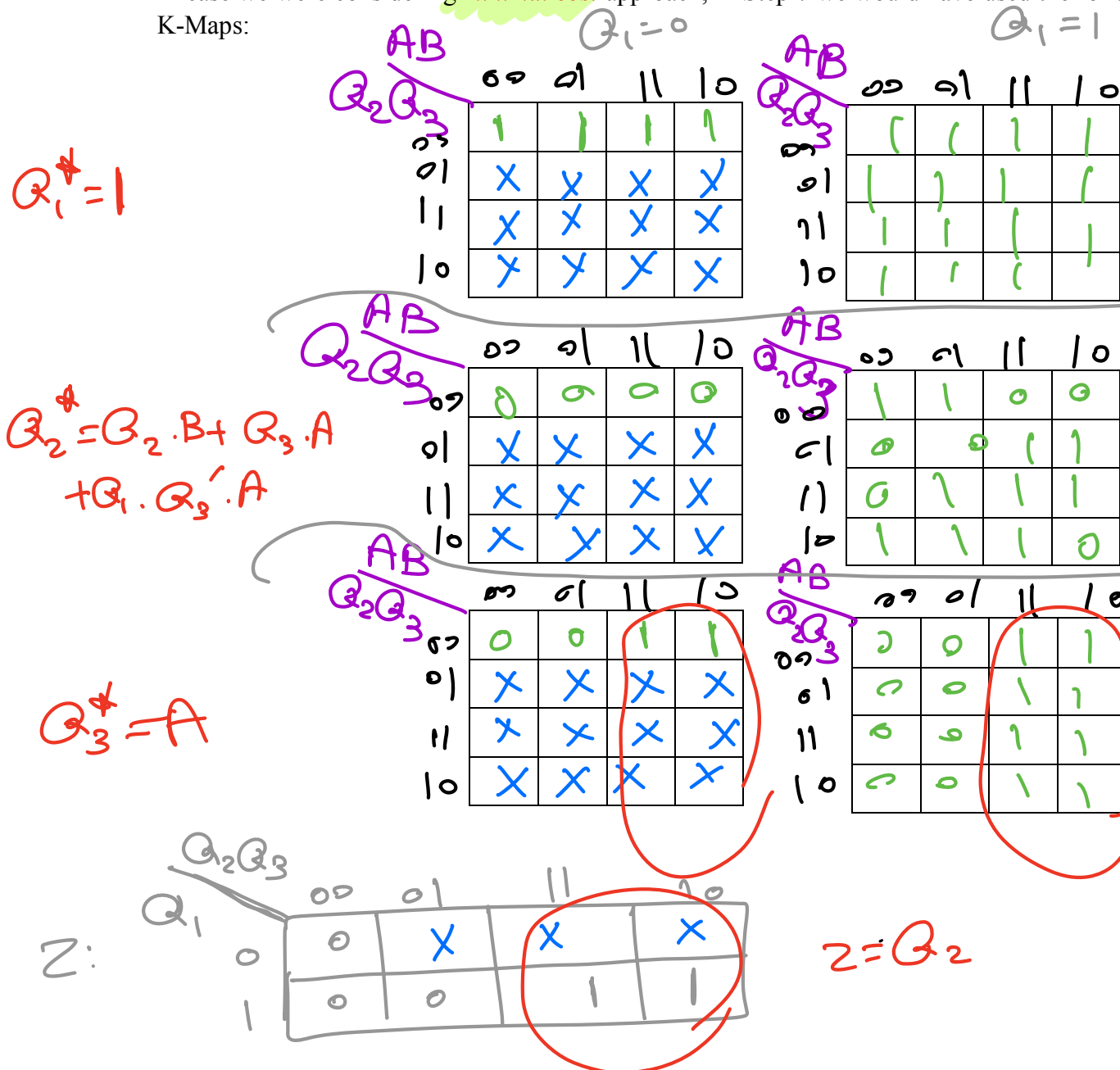
In case we were considering *minimal cost* approach, in Step 7 we would have used the following K-Maps:



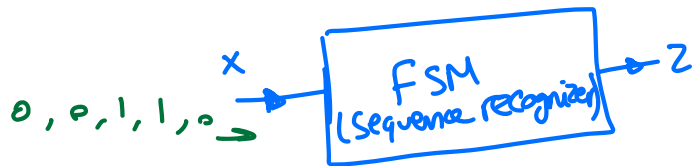**Example:** A "sequence recognizer" has one input  $X$  and one output  $Z$ . It has **Reset** applied to the direct reset inputs on its flip-flops to initialize the state of the circuit to all zeros. The circuit is to recognize the occurrence of the sequence of bits **1101** on  $X$  by making  $Z$  equal to 1 when the previous three inputs to the circuit were **110** and current input is a **1**. Otherwise,  $Z$  equals 0.



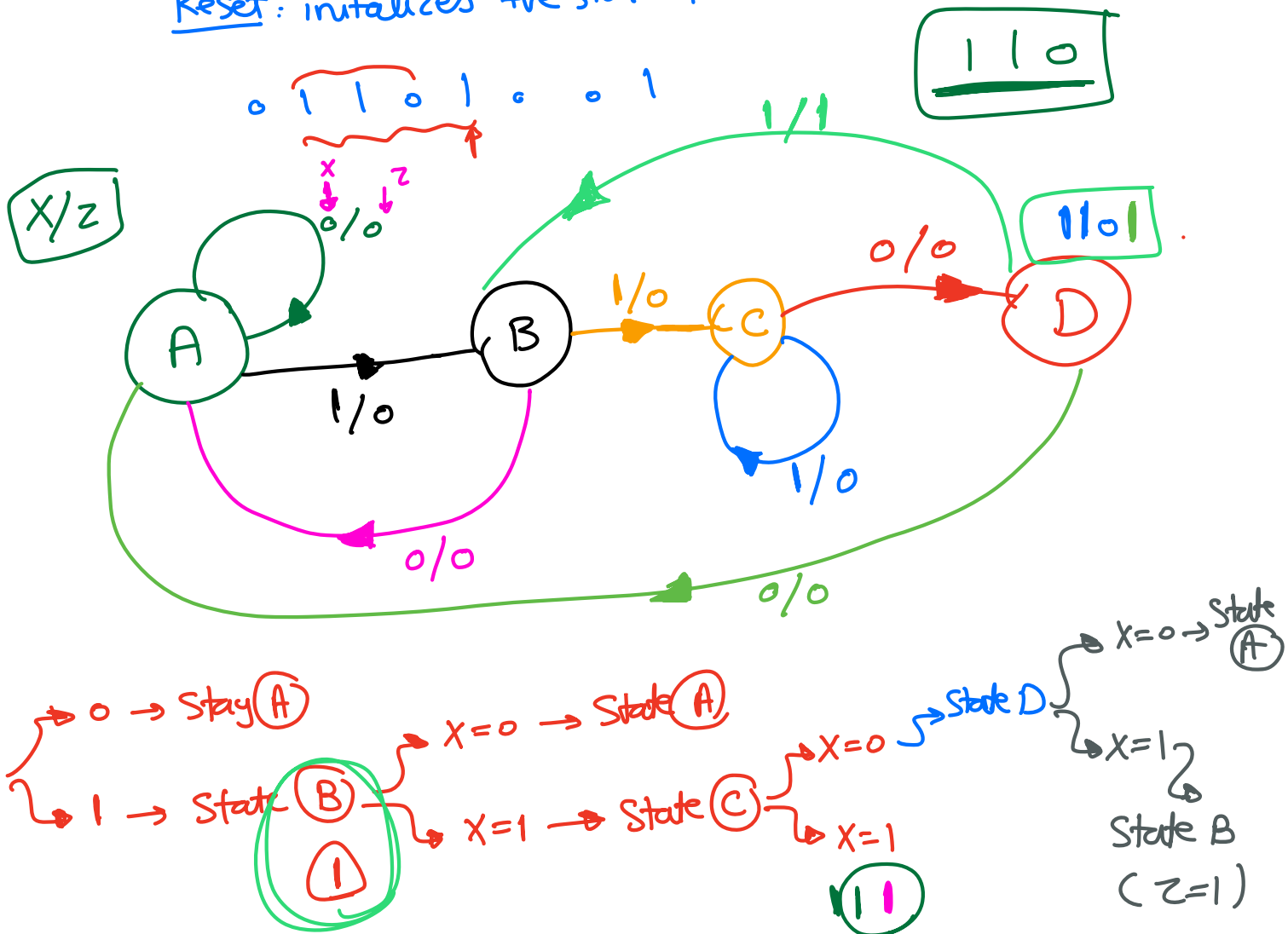Reset: initializes the state of the circuit to all zeros.





S	2		2	
	X=0	X=1	X=0	X=1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

$S^*$                        $X$

S	$Q_1$	$Q_2$
A	0	0
B	0	1
C	1	1
D	1	0

$X=0$		$X=1$	
0	0	0	1
0	0	1	1
1	0	1	1
0	0	0	1

$Q_1^*$                        $Q_2^*$                        $Q_1^* Q_2^*$

$Q_1, Q_2, X$

$Q_1 Q_2$		00	01	11	10
X	0	0	0	1	0
	1	0	1	1	0

$Q_1 Q_2$		00	01	11	10
X	0	0	0	0	0
	1	1	1	1	1

$$Q_1^* = Q_1 \cdot Q_2 + X \cdot Q_2$$

$$Q_2^* = X = D_2$$

$$= D_1$$

$Q_1 Q_2$		00	01	11	10
$X$	0	0	0	0	0
	1	0	0	0	1

$$Z = X \cdot Q_1 \cdot Q_2'$$

