
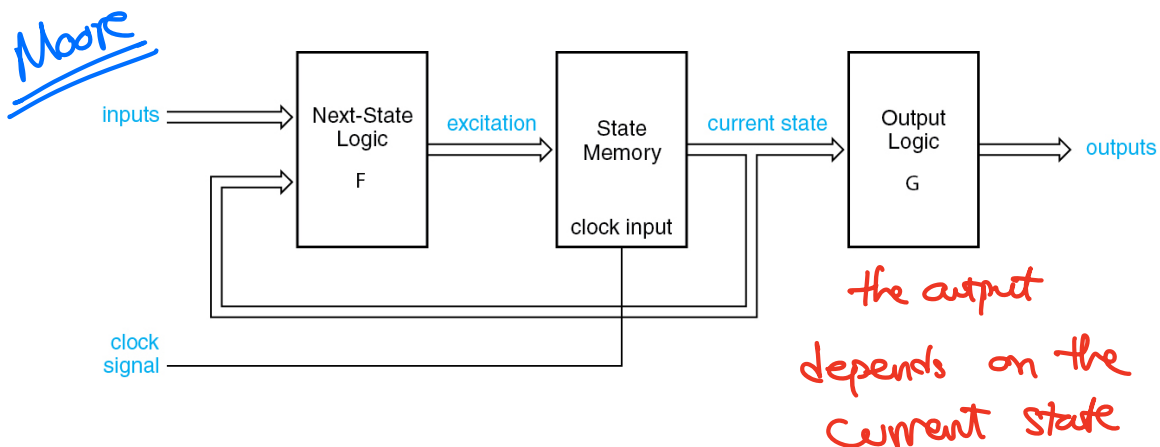


Analysis of Finite State Machines


Goal: Given a logic diagram, predict the behavior of the state machine, i.e., determine the next states and the output of the machine.

Tools:
 { state table
 { state diagram : { Circles : state
 { arcs : transitions between states


State Machines:

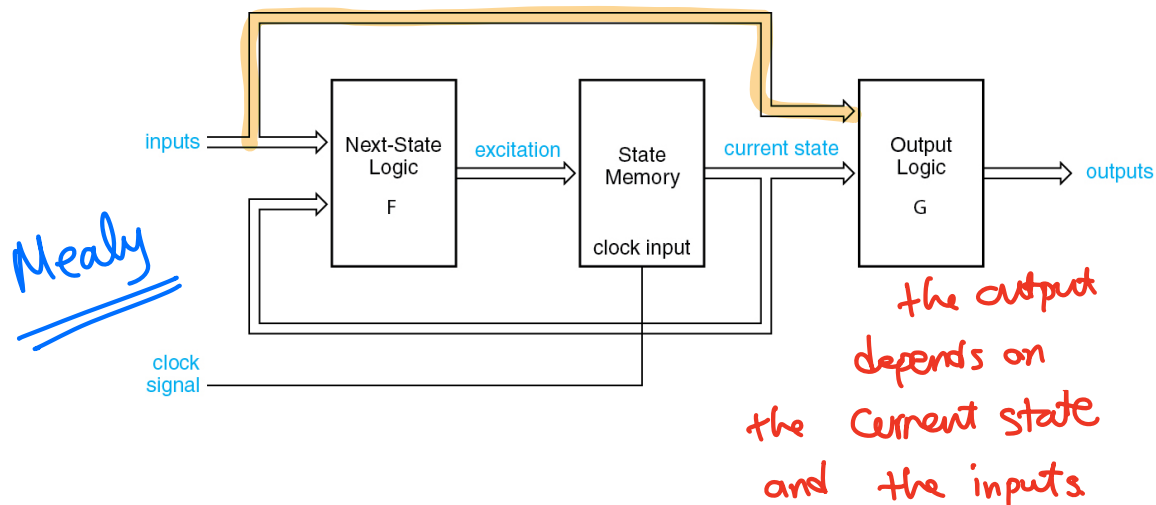


Examples:

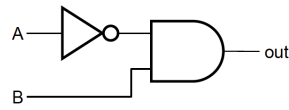

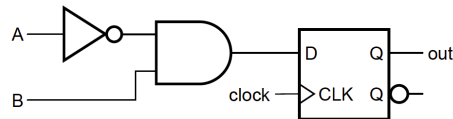Combinational
Circuit
(No clock, No memory)
this is not a sequential
Circuit.



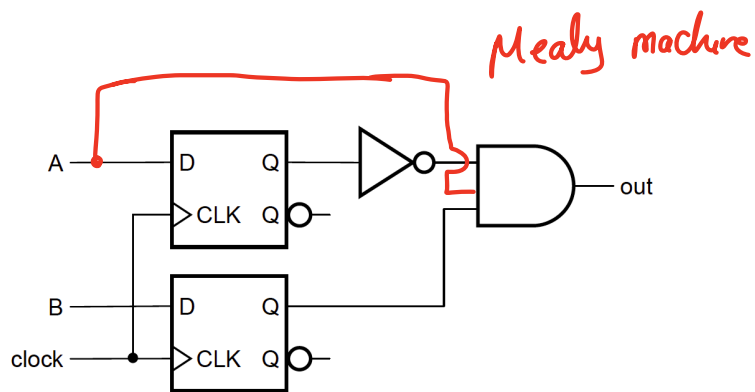Moore Machine
(No direct feeding of input to
the output)



Mealy machine
Moore Machine

Transition and State Tables

The diagram illustrates a 2-bit counter circuit. It features two D flip-flops, labeled Q0 and Q1, which serve as the state memory. The input EN (enable) is connected to the clock input of the Q0 flip-flop. The output of the Q0 flip-flop is connected to the clock input of the Q1 flip-flop. The next-state logic F, or "Excitation Logic", is implemented using a series of AND and OR gates. The output of this logic is connected to the D inputs of the flip-flops. The output logic G produces the output MAX, which is the sum of the outputs of the two flip-flops. Handwritten annotations in pink and orange highlight the excitation logic and the output logic, respectively. A pink oval encircles the entire circuit, and a pink arrow points to the output logic. An orange oval encircles the output logic, and an orange arrow points to the output MAX. The text "Excitation equations" is written in orange at the bottom right.

EN

Q0

Q1

CLK

Q0

Q1

MAX

Excitation equations

$$D_o = Q_o \cdot EN' + Q_o' \cdot EN$$

$$D_o = Q_o \cdot EN' + Q'_o \cdot EN$$

$$D_1 = Q_1 \cdot EN' + Q_0 \cdot Q'_1 \cdot EN + Q'_0 \cdot Q_1 \cdot EN$$

$$Q(t+\epsilon) = Q^* \quad \left\{ \begin{array}{l} Q_0^* = D_0 \\ Q_1^* = D_1 \end{array} \right.$$

$$Q(t+\epsilon) = Q^* \quad \left\{ \begin{array}{l} Q_0^* = D_0 \\ Q_1^* = D_1 \end{array} \right.$$

$$\begin{aligned} Q_0^* &= Q_0 \cdot EN' + Q_0' \cdot EN \\ Q_1^* &= Q_1 \cdot EN' + Q_0 \cdot Q_1' \cdot EN + Q_0' \cdot Q_1 \cdot EN \end{aligned}$$

$$\begin{aligned} Q_0^* &= Q_0 \cdot EN' + Q_0' \cdot EN \\ Q_1^* &= Q_1 \cdot EN' + Q_0 \cdot Q_1' \cdot EN + Q_0' \cdot Q_1 \cdot EN \end{aligned}$$

$$MAX = EN \cdot Q_1 \cdot Q_0$$

$$MAX = EN \cdot Q_1 \cdot Q_0$$

two state variables: Q_1, Q_0
 use the transition equations to find Q_1^*, Q_0^*

Transition and State Tables

	Q_1	Q_0
A	0	0
B	0	1
C	1	0
D	1	1

	EN	
	0	1
A	0 0	0 1
B	0 1	1 0
C	1 0	1 1
D	1 1	0 0

Q_1^*, Q_0^*

(State)


	EN	
	0	1
A	A	B
B	B	C
C	C	D
D	D	A

S^*
(Next State)

	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1


S^*, MAX
(Next state, output)

State Diagram

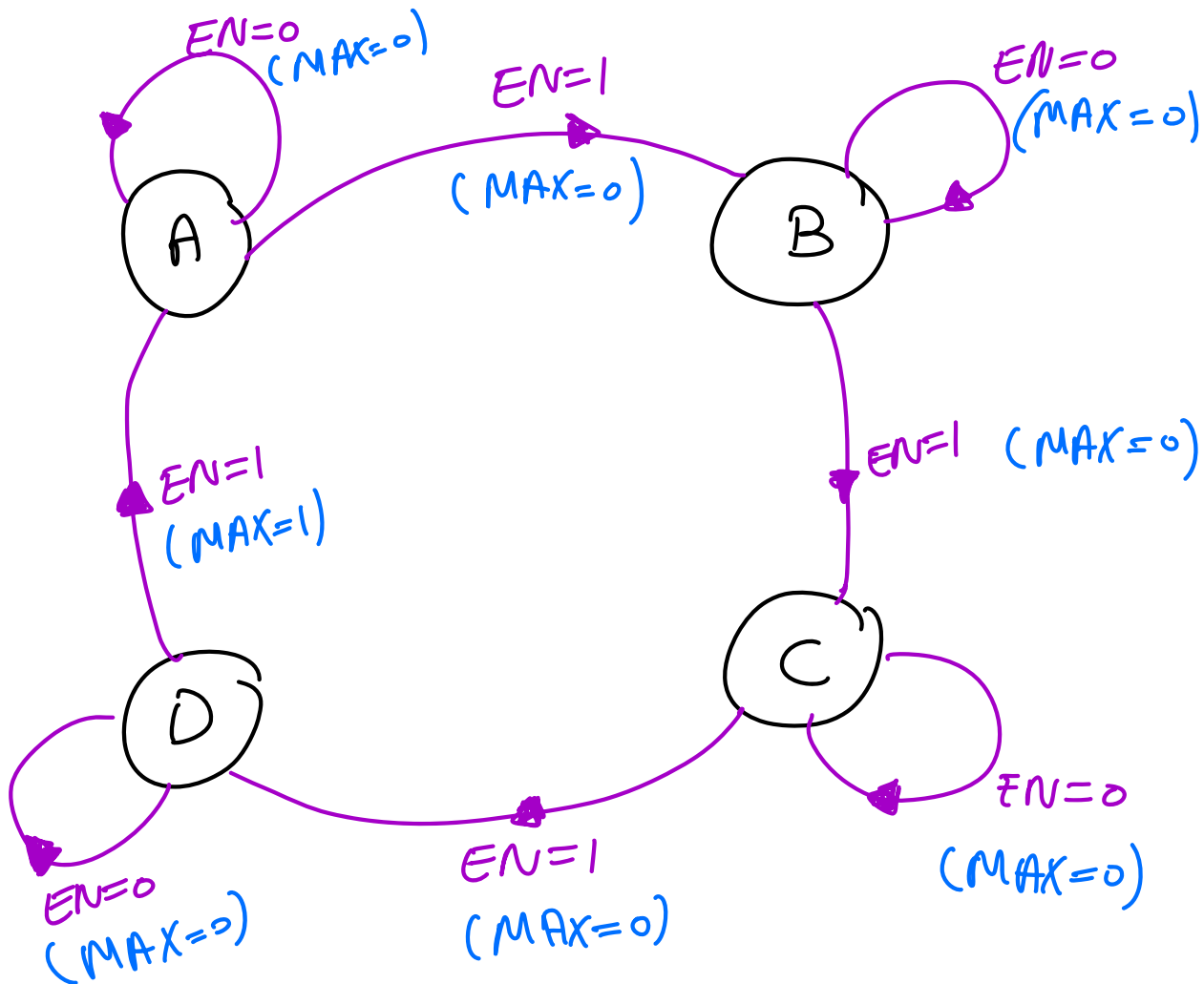

Mealy Machine

Example

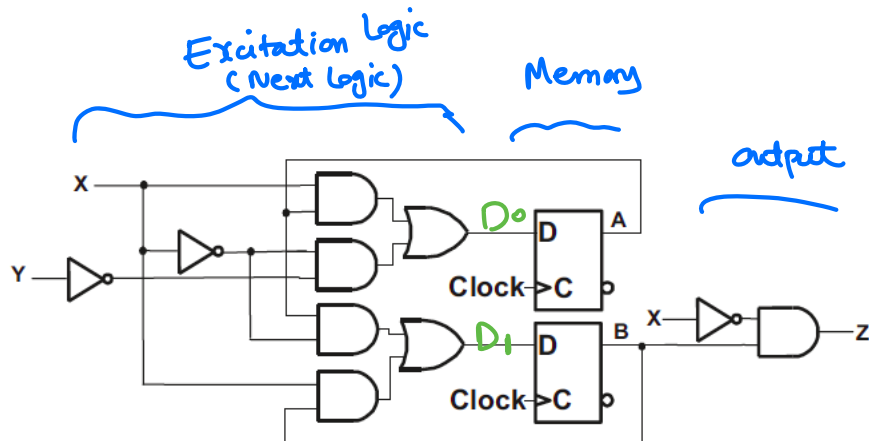


Mealy machine, $\begin{cases} 2 \text{ inputs: } x, y \\ 2 \text{ D-FF} \Rightarrow 2 \text{ state variables} \\ 1 \text{ output (z)} \end{cases}$

Excitation equations: $\begin{cases} D_0 = x \cdot A + x' \cdot y' \\ D_1 = x' \cdot A + x \cdot B \end{cases}$

Characteristic equations: $\begin{cases} A^* = D_0 \\ B^* = D_1 \end{cases}$

Transition equations: $\begin{cases} A^* = x \cdot A + x' \cdot y' \\ B^* = x' \cdot A + x \cdot B \end{cases}$

Output equation: $Z = x' \cdot B$

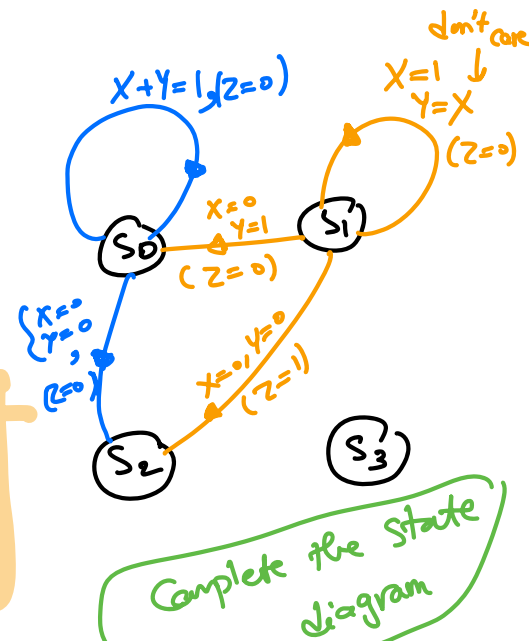


Complete the state diagram

	XY			
	00	01	10	11
S ₀	10	00	00	00
S ₁	10	00	01	01
S ₂	11	01	10	10
S ₃	11	01	11	11
	A*B*			

S	00	01	10	11
S ₀	S ₂ , 0	S ₀ , 0	S ₀ , 0	S ₀ , 0
S ₁	S ₂ , 1	S ₀ , 1	S ₁ , 0	S ₁ , 0
S ₂	S ₃ , 0	S ₁ , 0	S ₂ , 0	S ₂ , 0
S ₃	S ₃ , 1	S ₁ , 1	S ₃ , 0	S ₃ , 0
	S*, Z			

Example

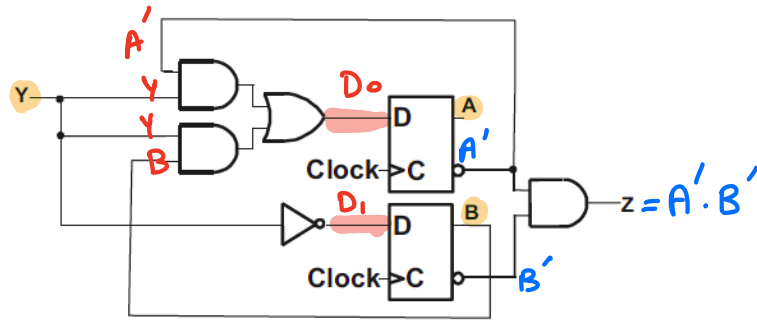

→ Moore Machine

→ one input: Y , two FFs → two state variables: A, B
 one output: Z

② Equations:

- Excitation equations: $\begin{cases} D_0 = (A' \cdot Y) + (Y \cdot B) \\ D_1 = Y' \end{cases}$
- Transition equations: $\begin{cases} A^* = (A' \cdot Y) + (Y \cdot B) \\ B^* = Y' \end{cases}$
- Output equations: $Z = A' \cdot B'$

	A	B
S_0	0	0
S_1	0	1
S_2	1	0
S_3	1	1


Y	0	1
S_0	01	10
S_1	01	10
S_2	01	00
S_3	01	10


S
 S_0
 S_1
 S_2
 S_3

Y	0	1
S_0	$S_1, 1$	$S_2, 1$
S_1	$S_1, 0$	$S_2, 0$
S_2	$S_1, 0$	$S_0, 0$
S_3	$S_1, 0$	$S_2, 0$

S^*, Z

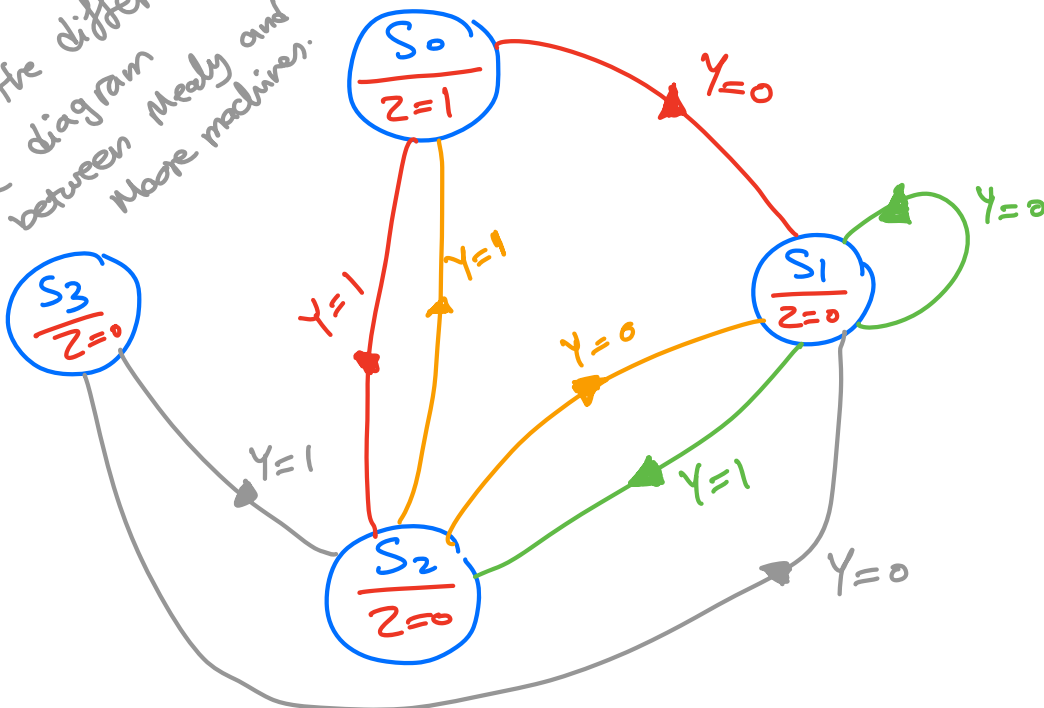Note the difference in state diagram between Mealy and Moore machines.



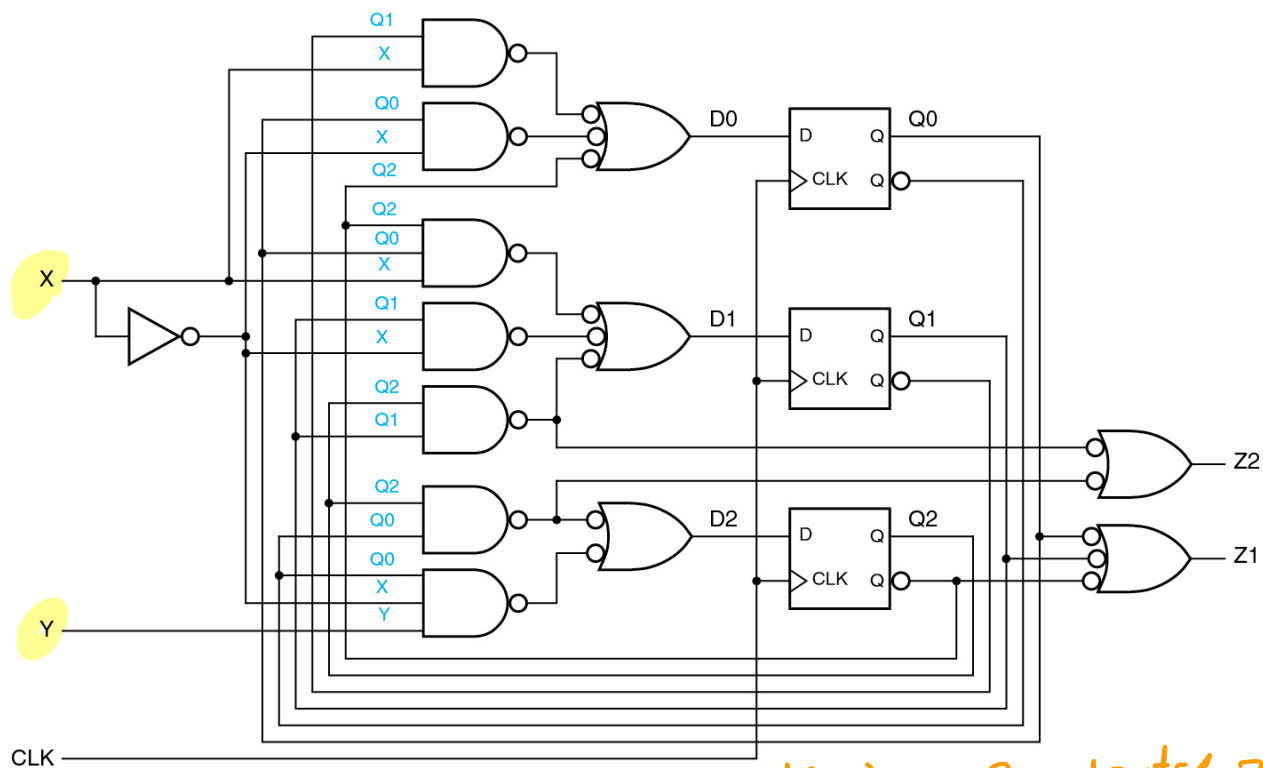

two inputs (X,Y), 3 FFs: (3 state variables) , 2 outputs (Z₁, Z₂)
Q₀, Q₁, Q₂

(a)

	XY				
	00	01	10	11	Z ₁ Z ₂
Q ₂ Q ₁ Q ₀	000	001	010	001	10
	001	001	011	011	10
	010	010	110	000	00
	011	011	010	010	11
	100	101	101	101	10
	101	001	001	001	11
	110	111	111	111	11
	111	011	011	011	11
	Q ₂ * Q ₁ * Q ₀ *				

(b)

	XY				
	00	01	10	11	Z ₁ Z ₂
S	A	E	B	B	10
A	B	B	D	D	10
B	C	G	A	A	10
C	D	D	C	C	00
D	F	F	F	F	11
E	B	B	B	B	10
F	H	H	H	H	11
G	D	D	D	D	11
H	S*				