

# Sequential Logic

Dov Kruger

Department of Electrical and Computer Engineering  
Rutgers University

October 29, 2024



# Kinds of Logic

- Combinational Logic: outputs depend only on the current inputs
- Sequential Logic: outputs depend on the current inputs and previous state
- State: the memory of the circuit
- Latches and flip-flops are the basic memory elements
- We have learned how to build memory using D-type Flip-Flops
- Now, it's time to learn to build them



# Overview of Sequential Logic

- Sequential logic circuits have memory
- Output depends on both current inputs and previous state
- Key components: latches and flip-flops
- Used for storing information and creating state machines
- Essential for creating registers, counters, and memory elements



# Types of Sequential Logic Elements


- Latches (Level-triggered)
  - SR Latch (Set-Reset)
  - D Latch (Data)
- Flip-Flops (Edge-triggered)
  - JK Flip-Flop
  - D Flip-Flop
  - T Flip-Flop (Toggle)
- Special configurations
  - Primary/Secondary Flip-Flop (formerly Master-Slave)
  - Edge-Triggered Flip-Flop implementations



# SR Latch Active High (NOR Implementation)

- Simplest form of latch
- Two inputs: Set ( $S$ ) and Reset ( $R$ )
- Two outputs:  $Q$  and  $Q'$  (complement of  $Q$ )
- Disadvantage: Undefined state when  $S = R = 1$


S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	X	X

 

# SR Latch Active Low (NAND Implementation)

- Same two inputs: Set ( $\overline{S}$ ) and Reset ( $\overline{R}$ )
- Two outputs:  $Q$  and  $Q'$  (complement of  $Q$ )
- Disadvantage: Undefined state when  $\overline{S} = \overline{R} = 1$

S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	X	X

 

# Gated SR Latch

- Similar to SR latch but with an additional Enable input ( $E$ )
- Two inputs: Set ( $S$ ) and Reset ( $R$ )
- Two outputs:  $Q$  and  $Q'$  (complement of  $Q$ )
- When Enable ( $E$ ) is high, the latch behaves like a regular SR latch
- When Enable ( $E$ ) is low, the latch holds its previous state regardless of  $S$  and  $R$  inputs
- Eliminates the problem of asynchronous changes in  $S$  and  $R$  inputs


$E$	$S$	$R$	$Q$	$Q'$
0	X	X	$Q$	$Q'$
1	0	0	$Q$	$Q'$
1	0	1	0	1
1	1	0	1	0
1	1	1	X	X

Youtube video animation:



[https://www.youtube.com/watch?v=peCh\\_859q7Q](https://www.youtube.com/watch?v=peCh_859q7Q)

# Gated SR Latch

 




# D Latch

- Eliminates the undefined state of SR latch
- Single data input (D) and enable input
- Output follows the input when enabled
- Holds the previous state when disabled
- Building block for more complex flip-flops

E	D	Q	Q'
0	X	Q	Q'
1	0	0	1
1	1	1	0



# D Latch

 


# JK Flip-Flop

- Improvement over SR flip-flop
- Two inputs: J (Set) and K (Reset)
- Clock input for synchronization
- Toggles output when  $J=K=1$
- No undefined states

J	K	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Q'	Q



# JK Flip-Flop

 


# T Flip-Flop

- Toggle flip-flop
- Single input T (Toggle) and clock input
- Implemented using JK flip-flop with  $J=K=T$
- Output toggles when  $T=1$  and clock edge occurs
- Maintains state when  $T=0$
- Useful for creating counters and frequency dividers

T	Q
0	Q
1	Q'




# T Flip-Flop

 

 
# D Flip-Flop (Rising Edge)

- Most commonly used flip-flop
- Single data input (D) and clock input
- Output changes only on clock edge (rising or falling)
- Stores the input state at the time of clock edge
- Used in registers and data storage elements
- This implementation may be a hack?


 
# T Flip-Flop

- Toggle flip-flop
- Single input T (Toggle) and clock input
- Output toggles when  $T=1$  and clock edge occurs
- Maintains state when  $T=0$
- Useful for creating counters and frequency dividers





# Edge-Triggered Flip-Flop

- Changes state only at a specific clock edge (rising or falling)
- Provides precise timing control
- Commonly used in synchronous digital systems
- Can be implemented as positive-edge or negative-edge triggered
- Most modern flip-flops are edge-triggered




# Counters: Introduction

- Counters are sequential circuits that count pulses
- They can count up, down, or both
- Implemented using flip-flops (usually T or JK flip-flops)
- Used in various applications: timers, frequency dividers, etc.



 
# Power of Two Counter

- Simplest form of counter
- Counts from  $0$  to  $2^n - 1$ , where  $n$  is the number of bits
- Implemented using T flip-flops
- Each flip-flop toggles at half the frequency of the previous one



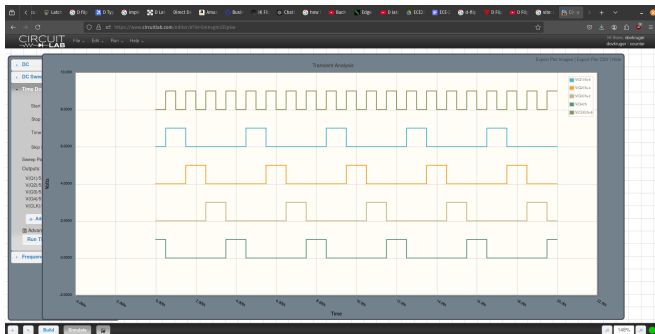
# 4-Bit Power of Two Counter: Operation

- Counts from 0000 to 1111 (0 to 15 in decimal)
- LSB toggles every clock cycle
- Each subsequent bit toggles when all previous bits are 1
- Automatically resets to 0000 after 1111



 
# State Machines: Introduction

- State machines are sequential circuits that transition between states based on inputs
- Start in a known start state
- Transition to other states based on input signals
- Used in various applications: control systems, communication protocols, etc.



 
# Implementing State Machines with D Flip-Flops

- State machines can be implemented using D flip-flops
- $n$  bits can represent a maximum of  $2^n$  different states
- Each flip-flop stores one bit of the state
- State transitions are determined by the input and current state


 
# State Machine Functions

- Two main functions in a state machine:
  - Output function: Defines the output for each state
  - Transition function: Defines how each state transitions to the next state based on inputs
  - Assign a unique number to each state
  - $bits = \lceil \log_2(\text{number of states}) \rceil$



# State Machine Example: Red Light Green Light

$D_0$	R	G
0	1	0
1	0	1

In this case, you can just toggle the state with a T flip-flop.

In general you need to determine for each state how to transition to the next state.





## Example: 2-bit State Machine

- State 00: Blue LED turns on
- State 01: Red LED turns on
- State 11: Green LED turns on
- State 10: All LEDs are off

$D_1$	$D_0$	R	G	B
0	0	0	0	1
0	1	1	0	0
1	1	0	1	0
1	0	0	0	0



## Example: Transitions for 2-bit State Machine

$Q_1$	$Q_0$	$D_1$	$D_0$
0	0	0	1
0	1	1	1
1	1	1	0
1	0	0	0

Now that you know what state you want to

be in, we can implement it



# State Machine Schematic

