

Digital Logic

Dov Kruger

Department of Electrical and Computer Engineering
Rutgers University

September 12, 2025



- Digital signals: 0 and 1
- Basis for all digital electronics
- Implemented using logic gates
- Combines signals to perform tasks



Why Digital?

- With an analog signal, difficult to distinguish signal and error
- With digital, a little noise can be ignored
- Digital signals are easier to store and process using computers
- Error detection and correction are more feasible with digital signals
- Digital systems are more scalable and compatible with modern technology



Combinatorial Logic Overview

- Output depends on input values
- No memory elements
- Built from basic gates
- Used in arithmetic and control circuits



Noise in Digital Signals

- Digital signals have noise
- Noise doesn't affect logic as long as it doesn't flip a bit
- Signal integrity depends on thresholds



Ringing and State in Digital Signals

- Digital is an abstraction
- Real-life signals have rise/fall time
- Ringing occurs after transitions
- Signal settles into a stable state



Trend in Voltage Levels

- Earliest digital: vacuum tubes (100V+)
- Early microprocessors: 5V
- Modern processors: 1.1V - 1.3V
- Power reduction with increased circuit density




Historical Voltage Levels

Computer	Year	Tech	Voltage	Size	Number of Devices	Power
ENIAC	1945	Tubes	150V - 300V	5 – 10 cm	18,000 tubes	150kW
IBM 7090	1959	Transistors	6V - 12V	1 – 2 cm	5,200	50kW
Cray-1	1976	IC	15V	5 μm	10,000 ICs	115kW
Intel 4004	1971	PMOS	15V	10 μm	2,300	1W
Intel 8086	1978	NMOS	5V	3 μm	29,000	2W
Pentium	1993	CMOS	3.3V	800 nm	3.1 $\times 10^6$	10W
Core i7-920	2008	CMOS	1.1V - 1.2V	45 nm	731 $\times 10^6$	95W
Core i7-7700K	2017	CMOS	1.2V	14 nm	1.2 $\times 10^9$	91W
Core i9-9900K	2020	CMOS	1.2V	14 nm	19 $\times 10^9$	125W
Apple M1	2020	CMOS	0.8V - 1.1V	5 nm	16 $\times 10^9$	15W
AMD Ryzen 9	2023	CMOS	0.8V - 1.1V	3 nm	16 $\times 10^9$	170W
Apple M4	2024	CMOS	0.7V - 1.0V	3 nm	25 $\times 10^9$	12W



NOT Gate

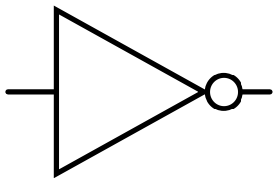


Boolean Algebra: \overline{A}

A	\overline{A}
0	1
1	0

It's hard to type the overline so there are other notations

$$\overline{A} = A' = \sim A$$




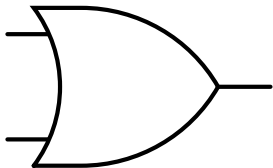

Boolean Algebra: $A + B$

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1


AND Gate

 

Boolean Algebra: $A \cdot B$

A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1


XOR Gate

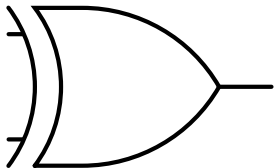

Boolean Algebra: $A \oplus B$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


NAND Gate

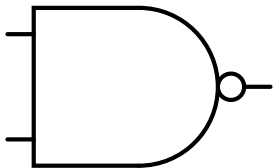

Boolean Algebra: $\overline{A \cdot B}$

A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate

 


Boolean Algebra: $\overline{A + B}$

A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

74LS Gate Sourcing Current

 
- 74LS gate can only source 0.4 mA
- Insufficient current for bright LED operation
- LED will barely glow due to limited current



Schematic showing 74LS gate sourcing an LED

74LS Gate Sinking Current

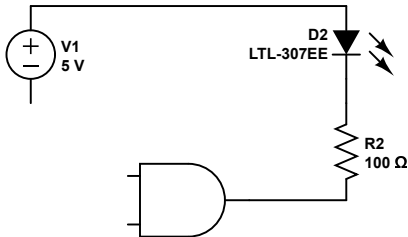
- 74LS gate can sink up to 16 mA
- Sufficient current to drive an LED partially




Schematic showing 74LS gate sinking an LED

Tying Outputs Together

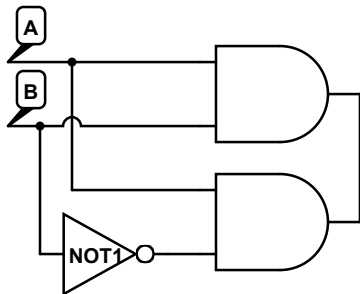
- You cannot wire together the outputs of two gates
- If the outputs are different values, it will create a short circuit
- This can damage the gates or other components



Sum of Products $F = AB + \overline{B}C$

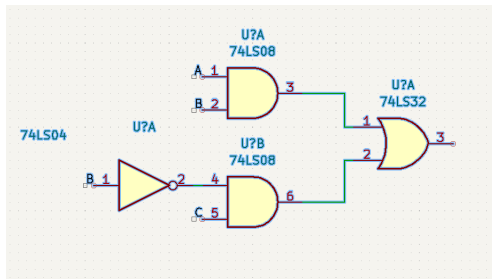

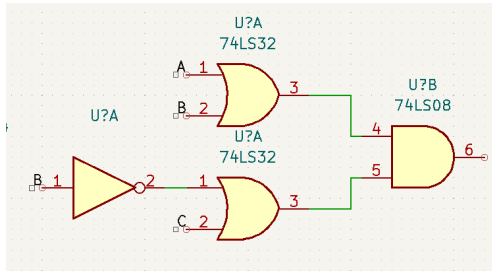Product of Sums $F = (A + B)(\overline{B} + C)$



Boolean Expression: $A + BC + A'C'$

Truth Table (Empty)

A	B	C	Output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



Boolean Expression Solution: $A + BC + A'C'$

Truth Table (Filled)

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Verilog Bitwise Operations

- `&` : AND
- `|` : OR
- `^` : XOR
- `~` : Bitwise NOT

```
module bitwise_operations;  
    reg a = 1;  
    reg b = 0;  
  
    reg r0 = a & b;  
    reg r1 = a | b;  
    reg r2 = a ^ b;  
    reg r3 = ~a;  
endmodule
```




Verilog Multiple Bits

```
module bitwise_operations;  
    reg [3:0] a = 4'b1010;  
    reg [3:0] b = 4'b1100;  
  
    reg [3:0] and_result = a & b;  
    reg [3:0] or_result = a | b;  
    reg [3:0] xor_result = a ^ b;  
    reg [3:0] not_result = ~a;  
endmodule
```



AND Gate Identities
 
$$A \cdot 1 = A \quad A \cdot 0 = 0 \quad A \cdot A = A \quad A \cdot \overline{A} = 0$$




Schematic for AND Gate Identities



OR Gate Identities
 
$$A + 1 = 1 \quad A + 0 = A \quad A + A = A \quad A + \overline{A} = 1$$




Schematic for OR Gate Identities



XOR Gate Identities
 
$$A \oplus 1 = \overline{A} \quad A \oplus 0 = A \quad A \oplus A = 0 \quad A \oplus \overline{A} = 1$$



Schematic for XOR Gate Identities




DeMorgan's Laws

- DeMorgan's First Law:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$


- DeMorgan's Second Law:
 
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$




Converting Sum of Products (SOP) to NAND

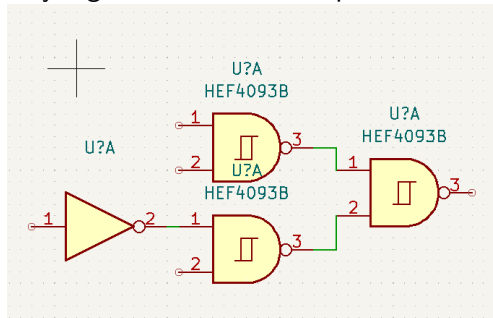Any logic circuit can be implemented using NAND




Constructing a 3-input OR gate

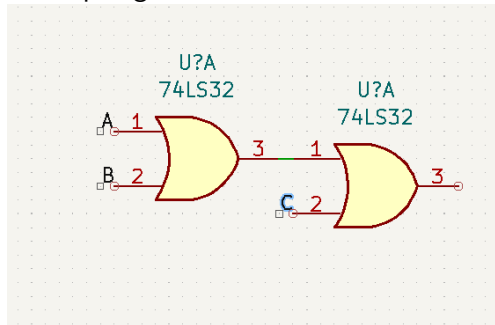A 3-input gate can be constructed from 2-input gates



Constructing a 3-input AND gate

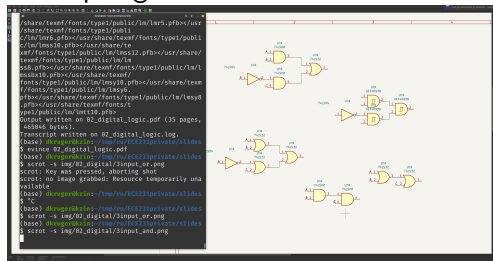A 3-input gate can be constructed from 2-input gates



Timing Hazards

- Timing delays can cause unexpected transient behavior.
- Steady-state analysis may miss potential glitches.
- A hazard occurs when a glitch is possible in a circuit.


Types of Hazards:

- Static-1 Hazard
- Static-0 Hazard
- Dynamic Hazard




Static-1 Hazard

 - Occurs with two input combinations that:
 - Differ in only one input variable
 - Both produce a 1 output
- A momentary 0 (glitch) can occur during the transition.



Static-0 Hazard

 - Occurs with two input combinations that:
 - Differ in only one input variable
 - Both produce a 0 output
- A momentary 1 (glitch) can occur during the transition.



Finding Static Hazards with Karnaugh Maps



Covering a Hazard



Hazard-Free Circuit



- Possibility of output changing multiple times
- Result of a single input transition
- Occurs with multiple paths
- Different delays from input to output

