

## 14:332:231-Digital Logic Design Assignment 4

1. A majority function is a function that has an output value of “1” if the number of 1s on its inputs is more than the number of 0s. Otherwise, its output value will be “0”. Find a Boolean expression for a 3-input majority function.
2. Design a 4-bit input combinational circuit that gives 3-bit binary output that is approximating the square root of the input number. For example, if the square root  $\geq 3.5$  it generates 4, and if the square root  $< 3.5$ , it generates 3.
3. Design a BCD to 7-Segment decoder (construct the truth table, plot the K-Maps for each output, and find the simplified sum-of-product function for each output).
4. Using five 2-to-4 decoders which also have “Enable” input, design a 4-to-16 decoder which also has an “Enable” input.
5. Build the following logic functions using **a)** one or more 74x138 decoder and AND/OR gates, and **b)** one or more 74x138 decoder and NAND/NOR gates.
  - i)  $F(X, Y, Z) = \sum_{X,Y,Z}(2,5,7)$
  - ii)  $F(X, Y, Z) = \prod_{X,Y,Z}(2,4,5,6,7)$
6. Design a 4-bit input priority encoder that follows the truth table below using basic logic gates (AND, OR, NAND, NOR, NOT).

D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>1</sub>	A <sub>0</sub>	IDLE
0	0	0	0	X	X	1
X	X	X	1	0	0	0
X	X	1	0	0	1	0
X	1	0	0	1	0	0
1	0	0	0	1	1	0

7. Build the Boolean function  $F(W, X, Y, Z) = \sum_{W,X,Y,Z}(1,3,4,11,12,13,14,15)$  using
  - a) a 8x1 multiplexer and external gates.
  - b) a 4x1 multiplexer and external gates.
  - c) two 3-to-8 decoders with enables and external gates with a maximum of 4 inputs.