

## 14:332:231-Digital Logic Design

### Assignment 3

**Due Date: 2:00 pm, 02/22/2023**

**1.** Optimize the following expressions in the form of sum-of-products using an appropriate K-map. Identify essential prime implicants.

a.  $F(X, Y, Z) = \sum_{X,Y,Z}(0, 2, 4, 6, 7)$

b.  $F(X, Y, Z) = X'Y' + XZ' + Y'Z + X'YZ'$

c.  $F(X, Y, Z, W) = \sum_{X,Y,Z,W}(0, 2, 4, 5, 8, 10, 11, 15)$

d.  $F(X, Y, Z, W) = \sum_{X,Y,Z,W}(1, 4, 5, 6, 10, 11, 12, 13, 15)$

e.  $F(X, Y, Z, W) = \sum_{X,Y,Z,W}(1, 5, 6, 7, 11, 12, 13, 15)$

**2.** Optimize the following expressions in the form of product-of-sums using an appropriate K-map.

a.  $F(X, Y, Z, W) = \sum_{X,Y,Z,W}(0, 1, 2, 8, 10, 12, 14, 15)$


b.  $F(X, Y, Z, W) = \prod_{X,Y,Z,W}(0, 2, 6, 7, 8, 9, 10, 12, 14, 15)$

**3.** Optimize the following expressions in the forms of sum-of-products and product-of-sums using an appropriate K-map.

a.  $F(X, Y, Z, W) = \sum_{X,Y,Z,W}(5, 6, 11, 12), d(X, Y, Z, W) = \sum_{X,Y,Z,W}(0, 1, 2, 9, 10, 14, 15)$

b.  $F(X, Y, Z, W) = \prod_{X,Y,Z,W}(3, 4, 6, 11, 12, 14), d(X, Y, Z, W) = \sum_{X,Y,Z,W}(0, 1, 2, 7, 8, 9, 10)$

 4. In the following circuit, the NOR gates have propagation delay of  $t = 0.073$  ns and the inverter has a propagation delay of  $t = 0.048$  ns. Find the propagation delay of the longest path through the circuit.



5. For the following logic expressions, find all of the static hazards in the corresponding two-level AND-OR circuit using a K-Map, and design a hazard-free circuit that realizes the same logic function:

a.  $F(X,Y,Z) = X.Y + X'Z'$

b.  $F(W,X,Y,Z) = W'X + Y'Z + W'XYZ + WXYZ'$

6. Using a truth table, find the expression of the sum-of-products and the AND-OR circuit realization for a) a 2-input XOR gate, and b) a 2-input XNOR gate.

7. Using K-Maps design a logic circuit that accepts the binary input  $a_4a_3a_2a_1a_0$ , and generates an output in the form of  $b_1b_0$ . In this circuit if the input is "1" (that is  $a_4a_3a_2a_1a_0 = 00001$ ) or if it is a prime number other than 2, the output should be  $b_1b_0 = 01$ . If the input is an even number, the output should be  $b_1b_0 = 10$ . In other cases the output can be  $b_1b_0 = 00$  or  $b_1b_0 = 11$ . Realize this circuit using only NAND gates.