


Binary Adders and Subtractors

Outline:

- Half Adder
- Full Adder
- Ripple Carry Adder
- Carry-Lookahead (CLA) Adder
- 74x283 4-bit Adder
- 16-bit Group-ripple Adder
- Subtractor

Half Adder (HA): Adds 2 bits. Has 2 inputs and 2 outputs.


X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
CO HS	0 0	0 1	0 1	1 0

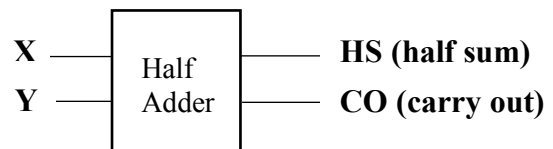

Constructing the truth table and finding Boolean expressions for HS and CO:


X	Y	HS	CO
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$HS = X \oplus Y$
 $CO = X \cdot Y$

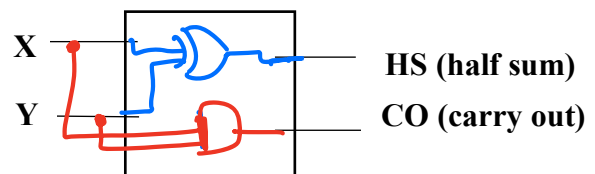

Full Adder (FA): Adds 3 bits. Has 3 inputs and 2 outputs.

Cin (carry in)	
+ X	
+ Y	
Cout	S

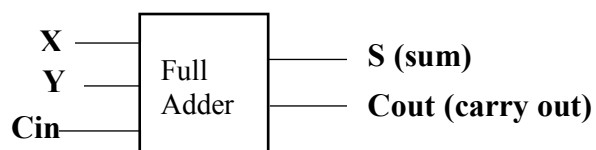

Constructing the truth table for FA and finding Boolean expressions for S and Cout:

Cin	X	Y	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



$C_{in} \backslash xy$	00	01	11	10
0		1		1
1	1		1	

$C_{in} \backslash xy$	00	01	11	10
0			1	
1		1	1	1

$S = X \oplus Y \oplus C_{in}$
 $C_{out} = X \cdot Y + C_{in} \cdot X + C_{in} \cdot Y$

$$\begin{aligned}
 C_{out} &= X \cdot Y + C_{in} (X + Y) = X \cdot Y + C_{in} [(X + Y) \cdot (X + X')] \\
 &= X \cdot Y + C_{in} [X + X' \cdot Y] = X \cdot Y + C_{in} \cdot X + C_{in} \cdot X' \cdot Y \\
 &= X \cdot Y + C_{in} \cdot X [Y + Y'] + C_{in} \cdot X' \cdot Y = \underline{X \cdot Y + C_{in} \cdot X \cdot Y} + C_{in} \cdot X' \cdot Y + C_{in} X' \cdot Y \\
 &= X \cdot Y [C_{in} + 1] + C_{in} [X \cdot Y' + X' \cdot Y] \\
 &= \underline{X \cdot Y} + \underline{C_{in} (X \oplus Y)}
 \end{aligned}$$

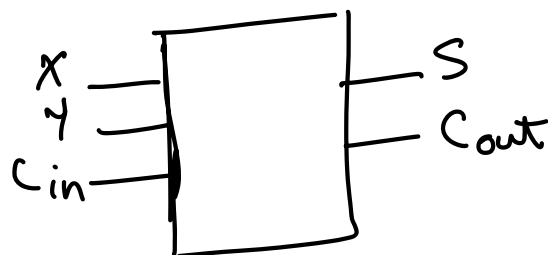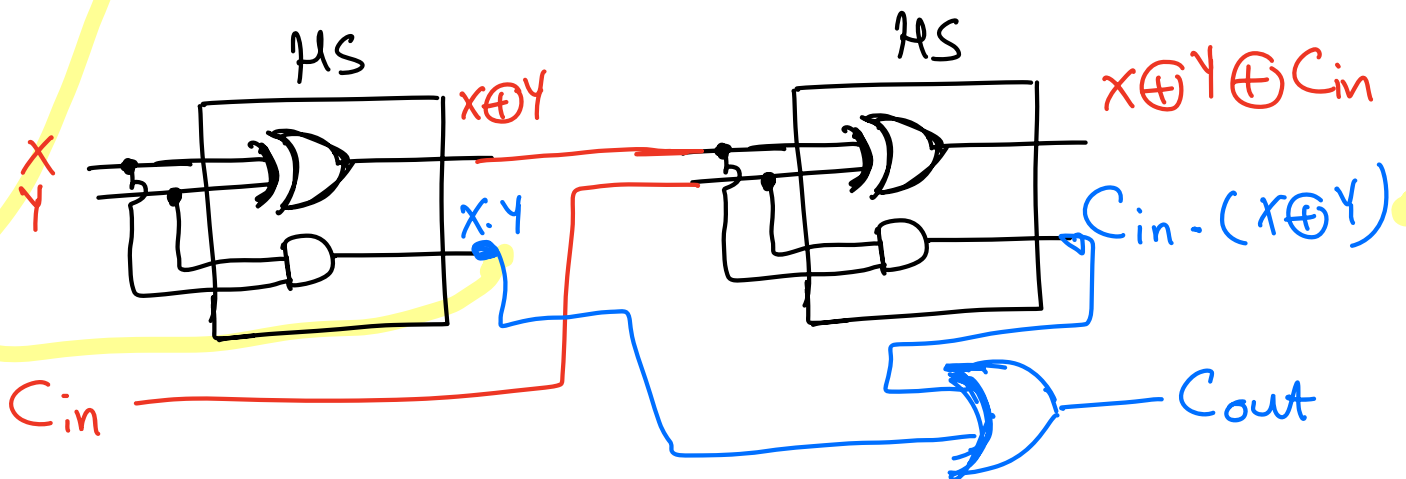
Implementing a Full Adder with Half Adders:




Ripple Carry Adder: cascading Full Adders, with the carry output from one Full Adder connected to the carry input of the next Full Adder.

A 4-bit Ripple Carry Adder:
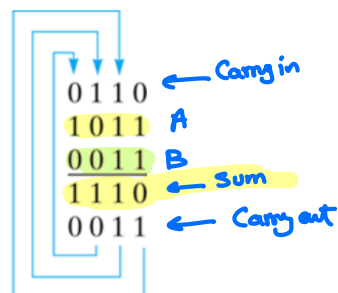
$$\begin{array}{r} a_3 \ a_2 \ a_1 \ a_0 \\ + \ b_3 \ b_2 \ b_1 \ b_0 \\ \hline c_4 \ s_3 \ s_2 \ s_1 \ s_0 \end{array}$$



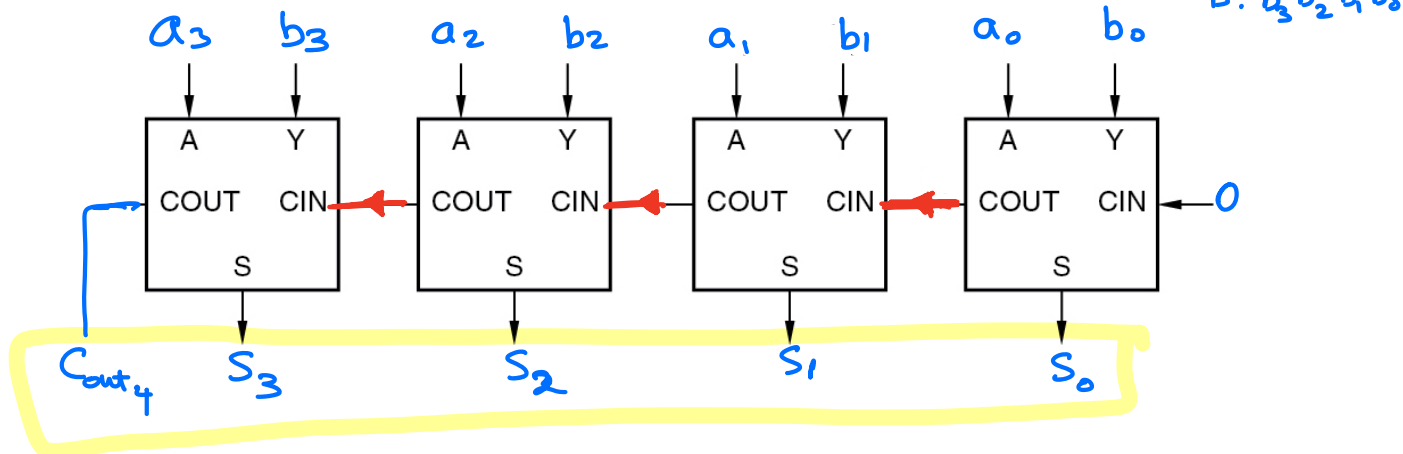
The input carry in the least significant position is 0. The output carry in each position is the input carry of the next-higher-order position.



A ripple adder is slow. In the worst case, a carry must propagate from the least significant Full Adder to the most significant one:

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$

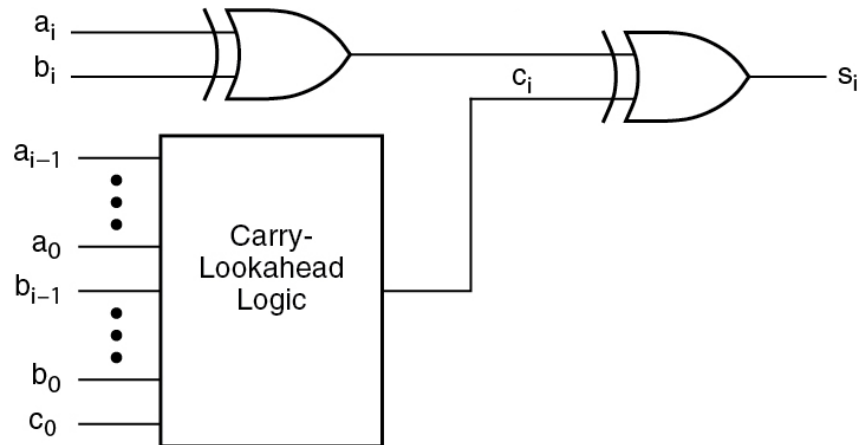Carry-Lookahead Adder: Calculates the carryout for each stage ahead of addition to speed up the computation, but it requires more complex circuits.



Some Definitions:


carry generate (g_i):

For a particular combination of inputs a_i and b_i , the adder stage i is said to *generate* a carry if it produces a $C_{out}=1$ (that is $C_{i+1}=1$), independent of what lower-order input bits (a_0, \dots, a_{i-1} and, b_0, \dots, b_{i-1}, c_0) are.

carry propagate (p_i):

For a particular combination of inputs a_i and b_i , the adder stage i is said to *propagate* a carry if it produces a $C_{out}=1$ (that is $C_{i+1}=1$), when $c_{in}=1$ (that is $c_i=1$).

For adder stage i :

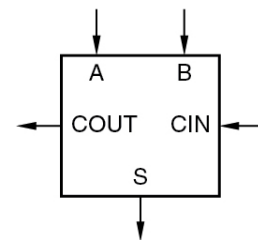


a_i	b_i	c_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 g_i &= a_i \cdot b_i \\
 p_i &= a_i \oplus b_i \\
 C_{i+1} &= g_i + C_i \cdot p_i \\
 &= a_i \cdot b_i + C_i \cdot (a_i \oplus b_i)
 \end{aligned}$$

(when consider the last term as generate)

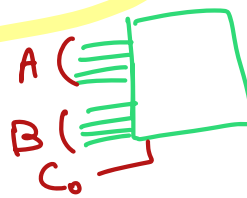If last term was considered as propagate,
then $P_i = a_i + b_i$



Carry equations in a 4-bit CLA adder:

$$C_1 = g_0 + C_0 \cdot P_0 = a_0 \cdot b_0 + C_0 \cdot (a_0 \oplus b_0)$$

$$C_2 = g_1 + C_1 \cdot P_1$$

$$= a_1 \cdot b_1 + [a_0 \cdot b_0 + C_0 \cdot (a_0 \oplus b_0)] \cdot (a_1 \oplus b_1)$$

$$C_3 = g_2 + P_2 \cdot C_2$$

$$= g_2 + P_2 \cdot (g_1 + P_1 \cdot g_0 + P_1 \cdot P_0 \cdot C_0)$$

$$= g_2 + P_2 \cdot g_1 + P_2 \cdot P_1 \cdot g_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0$$



$$C_4 = g_3 + P_3 \cdot C_3$$

$$= g_3 + P_3 \cdot (g_2 + P_2 \cdot g_1 + P_2 \cdot P_1 \cdot g_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0)$$


$$= g_3 + P_3 \cdot g_2 + P_3 \cdot P_2 \cdot g_1 + P_3 \cdot P_2 \cdot P_1 \cdot g_0 + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0$$

74x283 4-bit Adder:

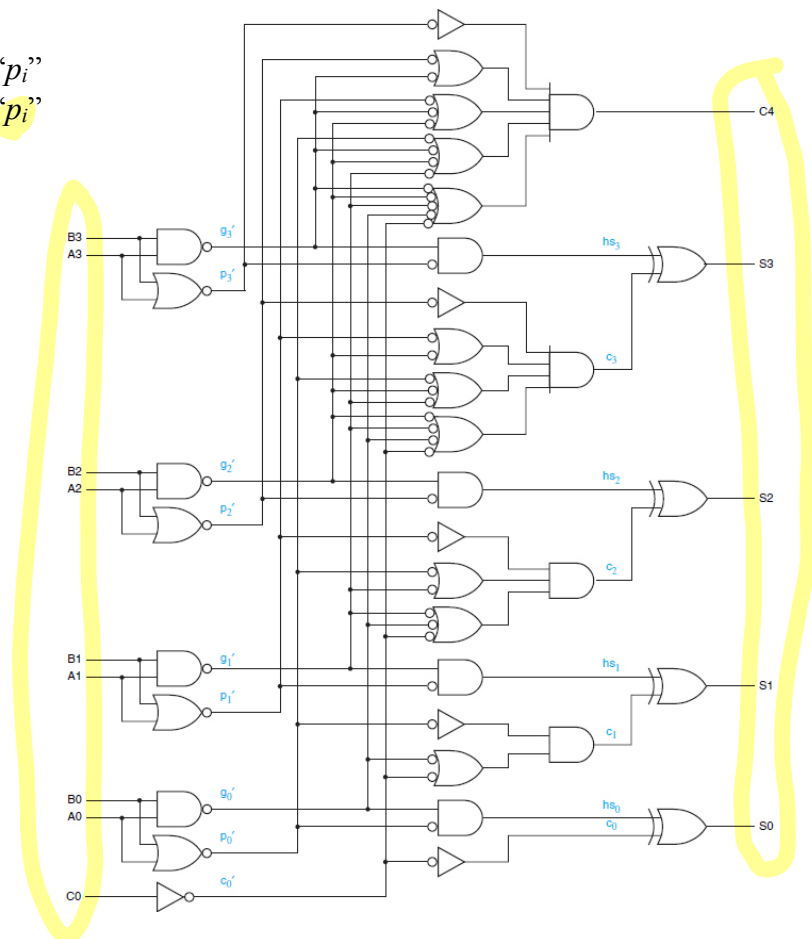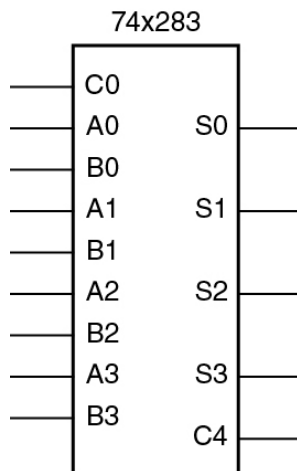- This is a 4-bit CLA adder.
- Generates active-low version for "g_i" and "p_i"
- Uses the "OR" version for implementing "p_i"



A more detailed look:

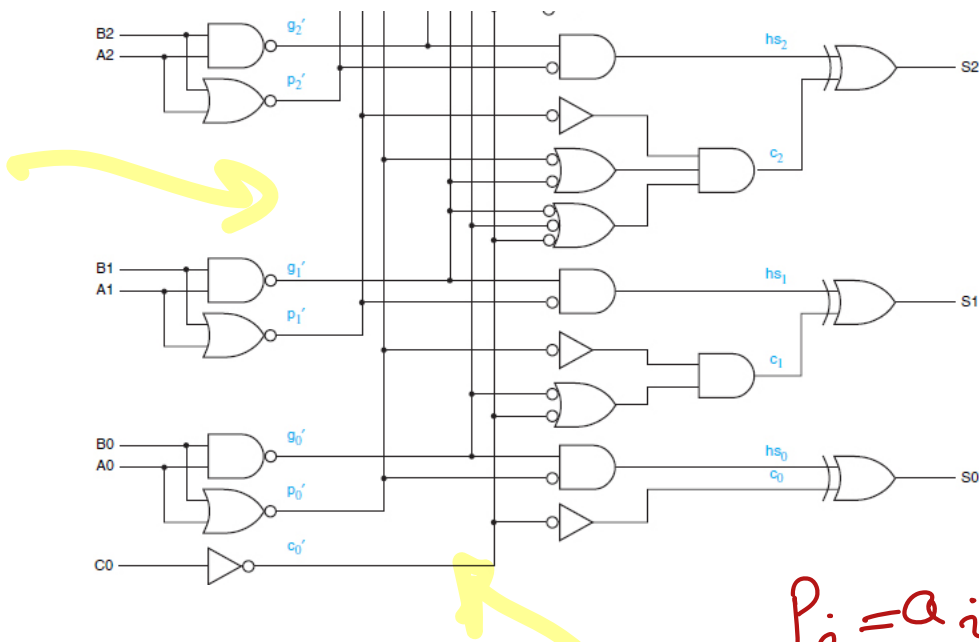

$$p_i = a_i + b_i$$


$$g_i = a_i \cdot b_i$$

Carry equations in a 74x283 adder:

$$\begin{aligned}
 c_1 &= p_0 \cdot (g_0 + c_0) \\
 c_2 &= p_1 \cdot (g_1 + c_1) \\
 &= p_1 \cdot (g_1 + p_0 \cdot (g_0 + c_0)) \\
 &= p_1 \cdot (g_1 + p_0) \cdot (g_1 + g_0 + c_0) \\
 c_3 &= p_2 \cdot (g_2 + c_2) \\
 &= p_2 \cdot (g_2 + p_1 \cdot (g_1 + p_0) \cdot (g_1 + g_0 + c_0)) \\
 &= p_2 \cdot (g_2 + p_1) \cdot (g_2 + g_1 + p_0) \cdot (g_2 + g_1 + g_0 + c_0) \\
 c_4 &= p_3 \cdot (g_3 + c_3) \\
 &= p_3 \cdot (g_3 + p_2 \cdot (g_2 + p_1) \cdot (g_2 + g_1 + p_0) \cdot (g_2 + g_1 + g_0 + c_0)) \\
 &= p_3 \cdot (g_3 + p_2) \cdot (g_3 + g_2 + p_1) \cdot (g_3 + g_2 + g_1 + p_0) \cdot (g_3 + g_2 + g_1 + g_0 + c_0)
 \end{aligned}$$

16-bit Group-Ripple Adder:

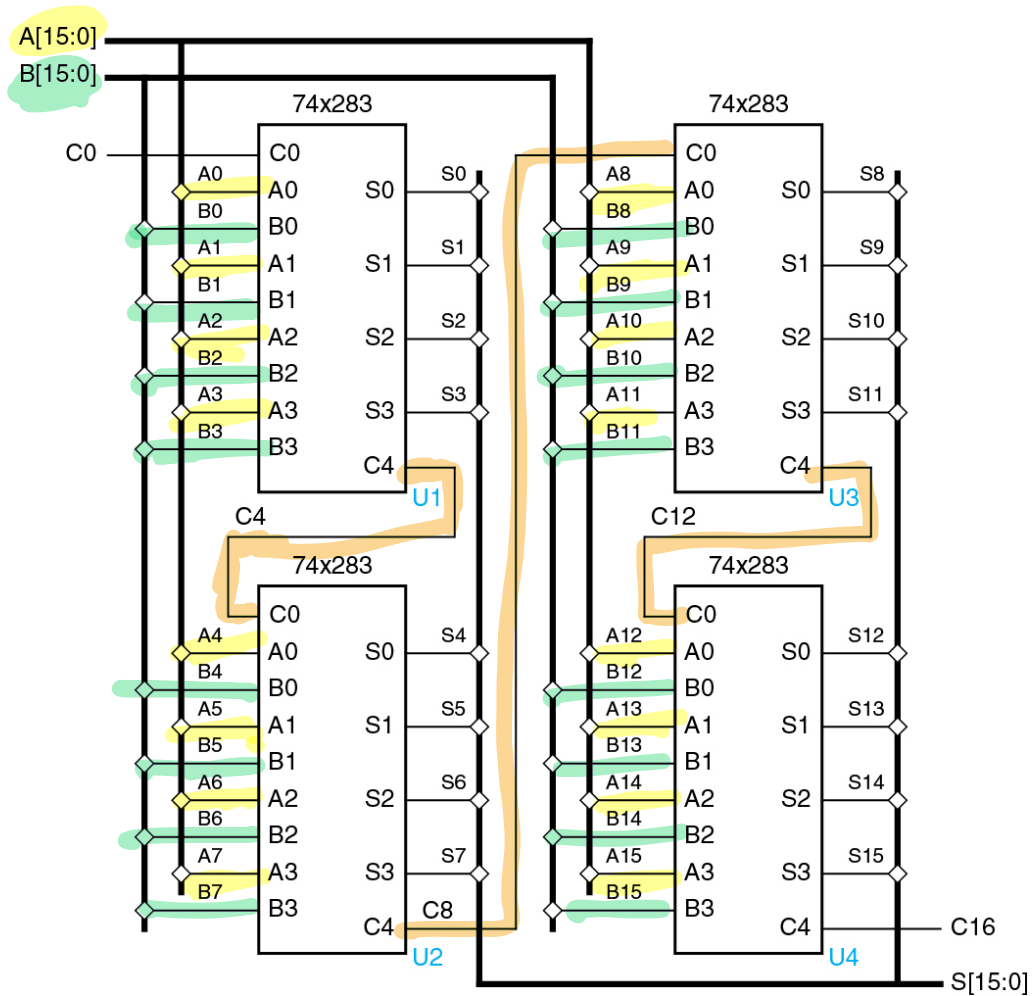
Building 16-bit Adder by cascading 4 4-bit CLA adders:




Two's-Complement Subtraction:

$$\begin{array}{r}
 A \quad a_3 a_2 a_1 a_0 \\
 - \quad b_3 b_2 b_1 b_0 \\
 \hline
 \end{array}
 \equiv
 \begin{array}{r}
 a_3 a_2 a_1 a_0 \\
 + \quad b'_3 b'_2 b'_1 b'_0 \\
 + \quad 1 \\
 \hline
 d_3 d_2 d_1 d_0
 \end{array}$$

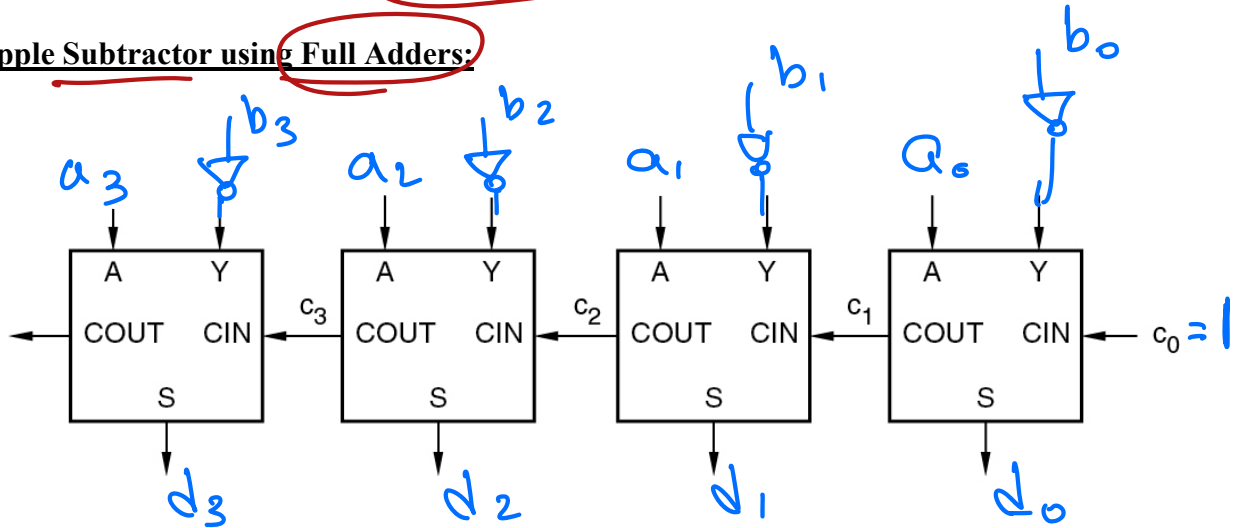4-bit Ripple Subtractor using Full Adders:



4-bit Ripple Adder/Subtractor:

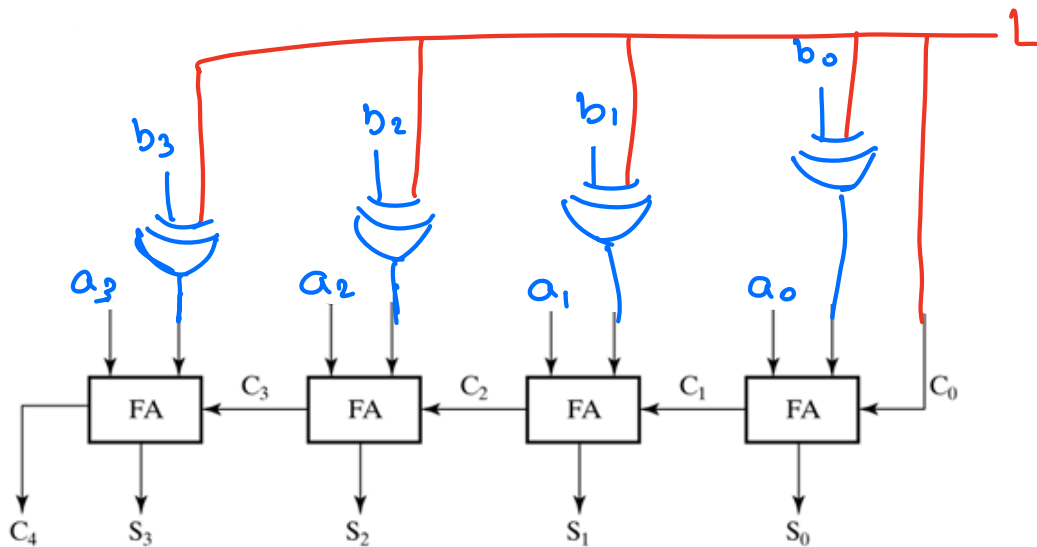

If $L=0$

$$\begin{array}{l}
 b_0 \oplus 0 = b_0 \\
 b_1 \oplus 0 = b_1 \\
 b_2 \oplus 0 = b_2 \\
 b_3 \oplus 0 = b_3
 \end{array}
 \equiv \text{addition}$$

If $L=1$

$$\begin{array}{l}
 b_0 \oplus 1 = b'_0 \\
 b_1 \oplus 1 = b'_1 \\
 b_2 \oplus 1 = b'_2 \\
 b_3 \oplus 1 = b'_3
 \end{array}
 \equiv \text{2's-complement Subtraction}$$

$C_0 = 1$

$$X \oplus Y = X \cdot Y' + X' \cdot Y$$

$$X \oplus 1 = X \cdot 0 + X' \cdot 1$$

$$= 0 + X'$$

$$= X'$$