

Arithmetic and Memory

Dov Kruger

Department of Electrical and Computer Engineering
Rutgers University

October 17, 2024




How do Computers do Arithmetic?

- This module describes how computers crunch numbers
- By the end you will be able to
 - Build a ripple carry adder
 - Calculate gate delays to know how long circuit takes
 - Design a faster carry look-ahead adder
 - Understand how multiplication works on a computer
 - Identify optimizations for multiplication and division (shift)
 - Learn what a flip-flop is and how it stores bits
 - Learn how to address memory




Half Adder

 - Half Adder: Adds two bits and outputs the sum and carry
- Inputs: A, B
- Outputs: Sum, Carry




Full Adder

 - Full Adder: Adds two bits and outputs the sum and carry
- Inputs: A, B, Carry
- Outputs: Sum, Carry
- Count the gate delays: 2
- 74LS gate delays typically 10ns
- modern gates in a CPU 10-20ps?




Ripple Carry Adder

 - Ripple Carry Adder: Adds two numbers using full adders
- Inputs: $A[3:0]$, $B[3:0]$
- Outputs: $\text{Sum}[3:0]$, Carry
- Count the gate delays: 4



Carry Look-Ahead Adder

 - Carry Look-Ahead Adder: Adds 4 bits and calculates the carry
- Inputs: $A[3:0]$, $B[3:0]$, Carry
- Outputs: $\text{Sum}[3:0]$, Carry
- Count the gate delays: 2



Multiplication

- Multiplication is repeated addition and shifting
- Long Multiplication example

$$\begin{array}{r} 64 \\ 986 \\ * 157 \\ \hline 6902 \\ 49300 \\ 986000 \\ \hline \end{array}$$

- Then add the results



Multiplication in Binary


01000001 (65)
x 00110001 (49)

01000001 (This is 65 shifted by 0)
01000001 (This is 65 shifted by 4)
010000010000 (This is 65 shifted by 5)
0000110011100001




D Type Flipflop

 - D Type Flipflop: Stores a bit
- Inputs: D, Clock
- Outputs: Q
- Every time the clock ticks, data is stored




D Type Flipflop Implementation

 * Before Simulating "Run Time Domain Simulation" to verify.
** WARNING: Do not destroy and paste anything from outside the box (especially the node labels) unless you "nest" in the three inputs together on all your flip flops.




Building a Register

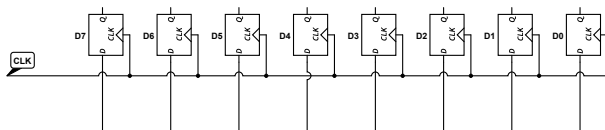
- Fastest computer memory is an array of flipflops
- Here is an 8-bit register



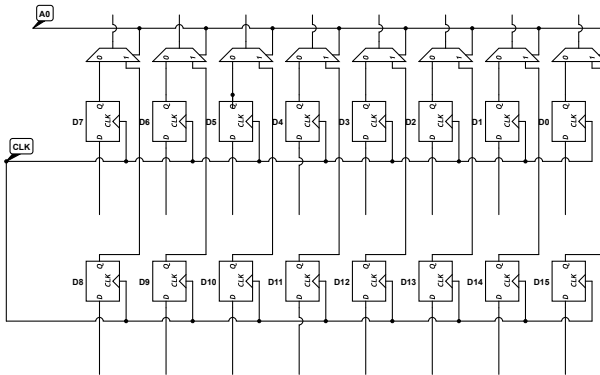Simplified Addressing Read Example: 1 bit



Simplified Addressing Write: 1 bit

 

Simulating Registers in Verilog

- First approach is a case statement
- However, this will get unwieldy many registers

```
module register(  
    input  [1:0] addr,  
    input  [7:0] data,  
    input  write,  
    output [7:0] out  
);
```



Simulating Registers in Verilog

```
reg [7:0] a, b, c, d
always @(posedge clk) begin
    if (write) begin
        case (addr)
            2'b00: a <= data;
            2'b01: b <= data;
            2'b10: c <= data;
            2'b11: d <= data;
        endcase
    end
    case (address)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        2'b11: out = d;
    endcase
end
```



end

- Arrays are ordered lists of variables

```
integer x; // one 32-bit integer  
integer y[10]; // 10 integers, from y[0] to y[9]  
integer z[3:0]; // 4 integers, from z[0] to z[3]  
reg [7:0] r[3:0]; // 4 8-bit registers, r[0] to
```



Register File using Arrays

```
module register_file(  
    input [1:0]  addr,  
    input [7:0]  data,  
    input  write ,  
    input  clk ,  
    output [7:0] out  
);  
    reg [7:0] registers [3:0];  
    always @(posedge clk) begin  
        if (write) begin  
            registers[addr] <= data;  
        end  
        out <= registers[addr];  
    end  
endmodule
```

