


Timing Hazards

Propagation Delay: In real circuits, when the input to a logic gate changes, the output does NOT change immediately.

This is because switching elements in the gate take time to react.

As a result, the change in the output is *delayed* with respect to the time that the input was changed.

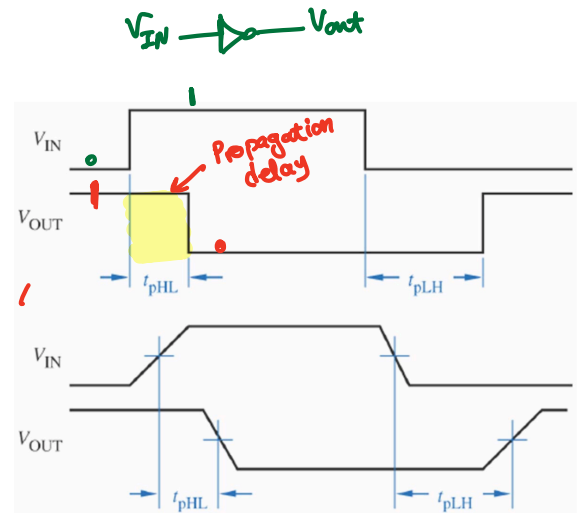This delay is referred to as the “*propagation delay*”.



Some Definitions:

Steady-State Behavior: output of logic circuit as a function of its inputs under the assumption that the *inputs have been stable* for a *long time*. “Long” here is relative to the delays in the circuit.

Transient Behavior: due to gate delays, logic circuits exhibit transient behavior. The transient behavior of a combinational logic circuit may *differ* from what is predicted by a steady-state analysis.


Glitch: is an *unwanted pulse* at the output of a combinational logic circuit (a *momentary change* in an output that should not have changed).

Hazard: A *circuit* with the *potential for a glitch* is said to *have a hazard*. A hazard is something intrinsic about a circuit; a circuit with hazard may or may not have a glitch depending on input patterns and the electric characteristics of the circuit.


Hazards occur in the output when *different paths from input to output* have *different propagation delays*.

Static Hazard: The *output* undergoes a *momentary transition* when it is *expected to remain unchanged*.


Static-1 Hazard:

 

Static-0 Hazard:

 


 Dynamic Hazard: The *output is supposed to change*, but it *changes multiple times in between*, before it settles to its new logic value.




Detection of Static Hazards & Designing Hazard-Free Circuits

Example:

 


$$F = BC + AC'$$

 

Assume each gate has propagation delay of t_p .

$$\begin{cases} A=1 \\ B=1 \\ C=1 \end{cases} \rightarrow f=1$$
 
$$\begin{cases} A=1 \\ B=1 \\ C=0 \end{cases} \rightarrow f=1$$



Observations:

- When representing a function as a Sum-of-Products (AND-OR) circuit, the AND gates correspond to the prime implicants of the K-Map.
- Change in the input " C " (from 1 \rightarrow 0) propagates to the output F along two paths with different delays. This difference has caused the glitch in the output.
- A hazard happened when there is a *transition* between *prime implicants* (i.e. between the AND gates).

Detection of Static-1 Hazards:

- A potential hazard exists when two adjacent 1-cells in a K-Map are NOT covered by a single product term (prime implicant) in the circuit.
- Note that two-level OR-AND circuits (based on POS) have no static-1 hazard.



Detection of Static-0 Hazards:

- A potential hazard exists when two adjacent 0-cells in a K-Map are NOT covered by a single sum term in the circuit.
- Note that two-level AND-OR circuits (based on SOP) have no static-0 hazard.

Approaches for Eliminating Hazards:

1. **Wait!** Evaluate the output at intervals that are longer than the maximum propagation delay in the circuit.
2. **Match propagation delays:** make sure propagation delays from input to output for different paths in the circuit are the same. In the example above, you could add a buffer in the top row. In practice, matching the propagation delays in different paths is difficult to achieve. *e.g. you could add a buffer gate before the top AND gate*
3. **Add redundant prime implicants:** find the prime implicant that covers all adjacent 1-cells, and add it as an extra product term to the function.

Example:

  

SOP

Example (Static-1 Hazard):

Yz \ wx				
	00	01	11	10
00		1	1	
01	1	1		
11	1	1	1	1
10			1	1

$$F(YZwx) = Z.W' + Y.W + Y'.Z'.X$$

$$\begin{matrix} Y'.W'.X \\ Y.Z \\ Z'.W.X \end{matrix}$$

Redundant Prime implicants that need to be added so the circuit stay static Hazard-free.

Yz \ wx				
	00	01	11	10
00		1	1	
01	1	1		
11	1	1	1	1
10			1	1

Example (Static-0 Hazard):

AB \ CD				
	00	01	11	10
00	0	0		
01	0	0	0	0
11			0	0
10	0	0		

$$(A+C)$$

$$(A'+D')$$

$$(B'+C'+D)$$

POS

$$F(A,B,C,D) = (A+C).(A'+D').(B'+C'+D)$$

AB \ CD				
	00	01	11	10
00	0	0		
01	0	0	0	0
11			0	0
10	0	0		

$$(C+D')$$

$$(A'+B'+C')$$

$$(A+B'+D)$$

Need to add $(C+D')$, $(A'+B'+C')$


$$(A+B'+D)$$

to $F(A,B,C,D)$

to eliminate Static-0 Hazard.

 Example (Dynamic Hazard):

If there are multiple paths from an input (or its complement) to the output, the circuit has a potential for a dynamic hazard. Analysis and elimination of dynamic hazards is a complicated process, and usually solved by computer programs.



$$\begin{array}{l} \left. \begin{array}{l} A=0 \\ B=0 \\ C=0 \end{array} \right\} \rightarrow \left. \begin{array}{l} A=0 \\ B=1 \\ C=0 \end{array} \right\} \\ F=1 \qquad \qquad F=0 \end{array}$$

