

# ECE231: Electronics Cheatsheet

Dov Kruger

## Basic Formulas

### Ohm's Law:

$$V = IR$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

### Series Resistance:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

### Parallel Resistance:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \text{ (for 2 resistors)}$$

### Capacitor Energy:

$$E = \frac{1}{2} CV^2$$

### Series Capacitance:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

### Parallel Capacitance:

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

### RC Circuit Charging:

$$V_C(t) = V_S(1 - e^{-t/\tau})$$

$$I(t) = \frac{V_S}{R} e^{-t/\tau}$$

### RC Circuit Discharging:

$$V_C(t) = V_0 e^{-t/\tau}$$

$$I(t) = -\frac{V_0}{R} e^{-t/\tau}$$

where  $\tau = RC$  (time constant)

## Passive Components

Resistor (US)



Resistor (IEC)



Capacitor



Electrolytic Cap



Battery



Voltage Source



Earth Ground



Signal Ground



LED



Diode



## Logic Gates

AND



OR



NOT



NAND



NOR



XOR



## Transistors

NPN BJT



PNP BJT



n-MOSFET



p-MOSFET



n-FET




p-FET




## IC Pinouts


7404 (Hex Inverter) 7408 (Quad AND)

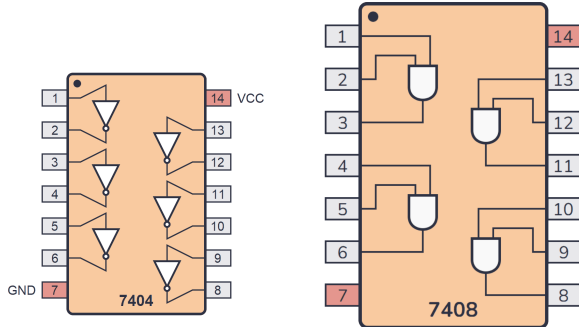


7432 (Quad OR)

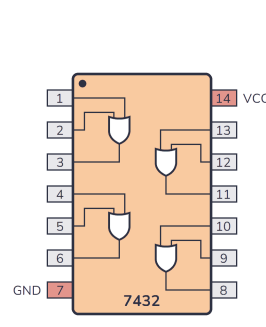


555 Timer

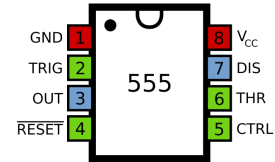

ATmega328 (DIP)

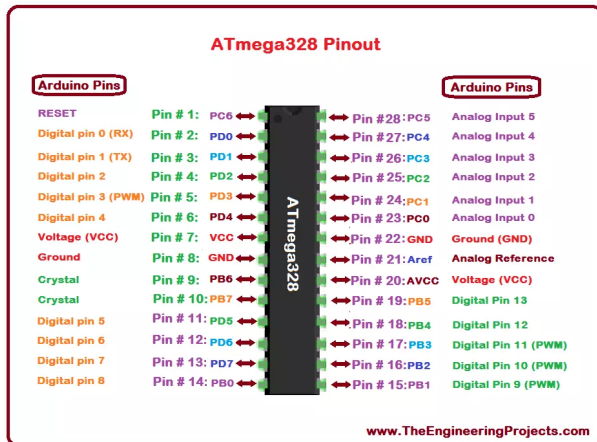

ATmega328 (Quad)

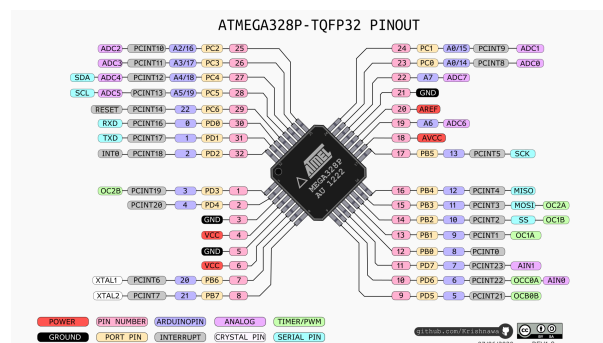

## Common Values

- **Resistor Colors:** Black(0), Brown(1), Red(2), Orange(3), Yellow(4), Green(5), Blue(6), Violet(7), Gray(8), White(9)
- **Standard Resistors:** 1.0, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 ( $\times 10^n$ )

## Power Supply

- **TTL Logic:** VCC = 5V, VSS = 0V
- **CMOS Logic:** VDD = 3.3V or 5V, VSS = 0V
- **Arduino:** 5V, 3.3V, GND